

Lecture 4


- Measurement of small voltages
 - Measurement of resistance

MEASUREMENT OF SMALL VOLTAGES


- *voltage has to be amplified before being measured*
- *input impedance has to be increased in some particular case*

For example



THERMOCOUPLE

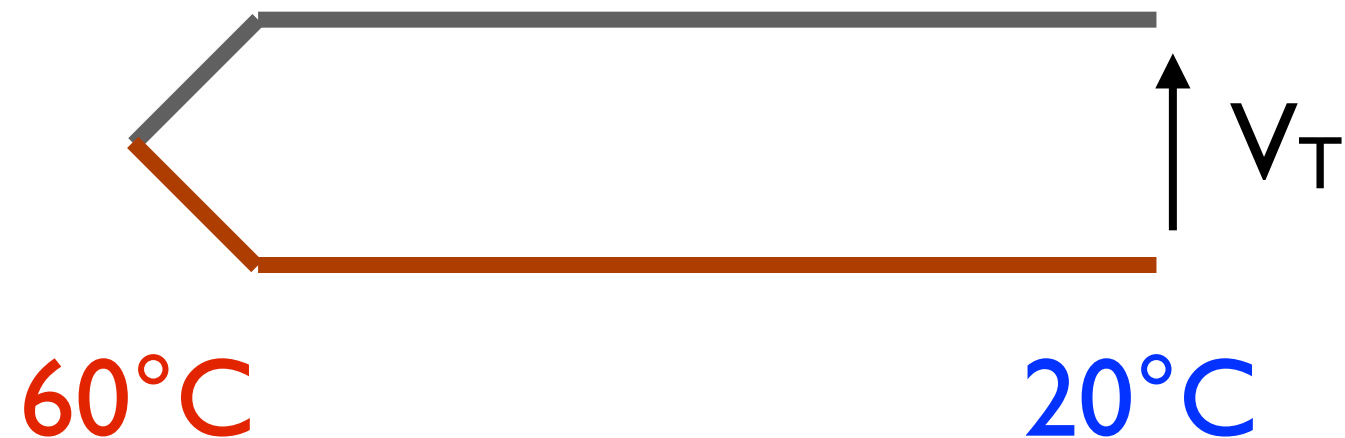
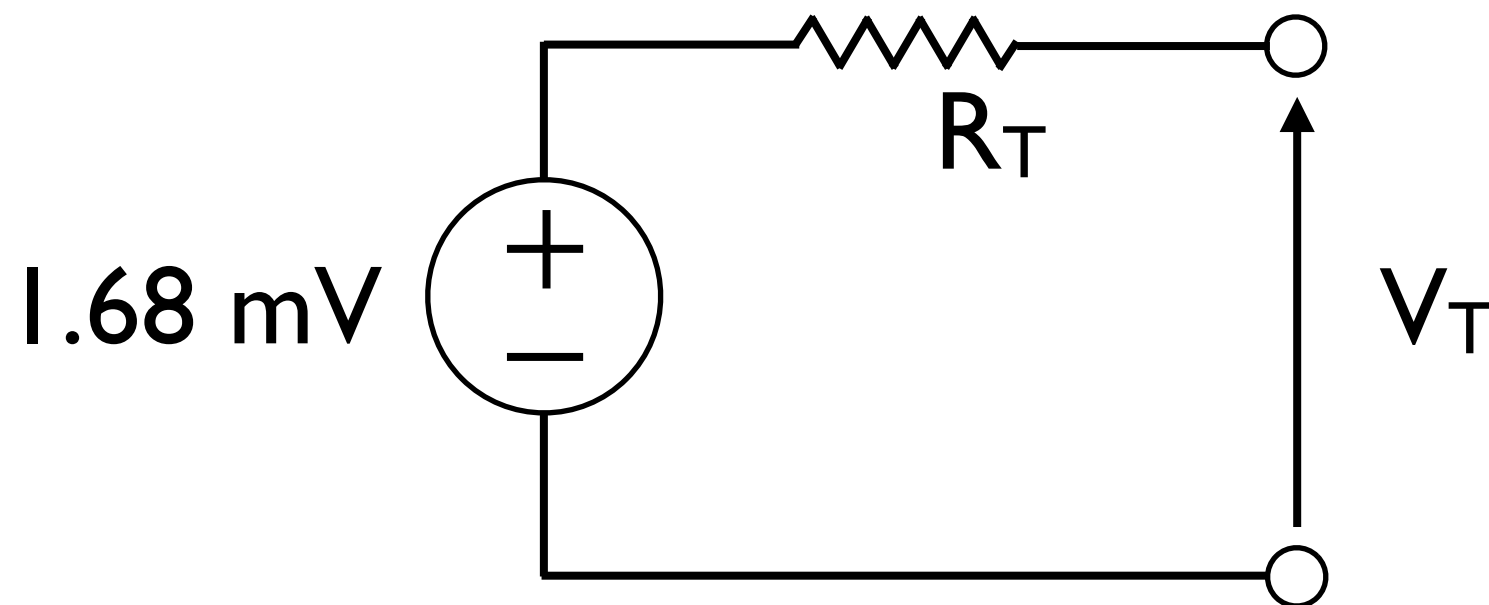
$$V_T = k \cdot \Delta T = 42 \mu\text{V/K} \cdot (60 - 20) = 1.68 \text{ mV}$$



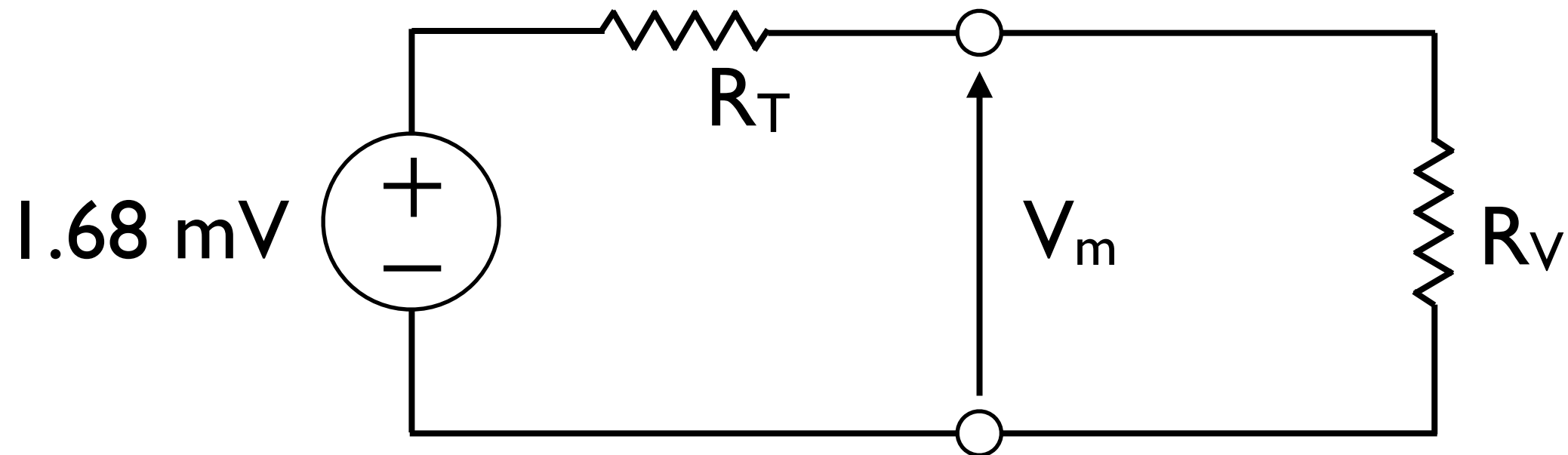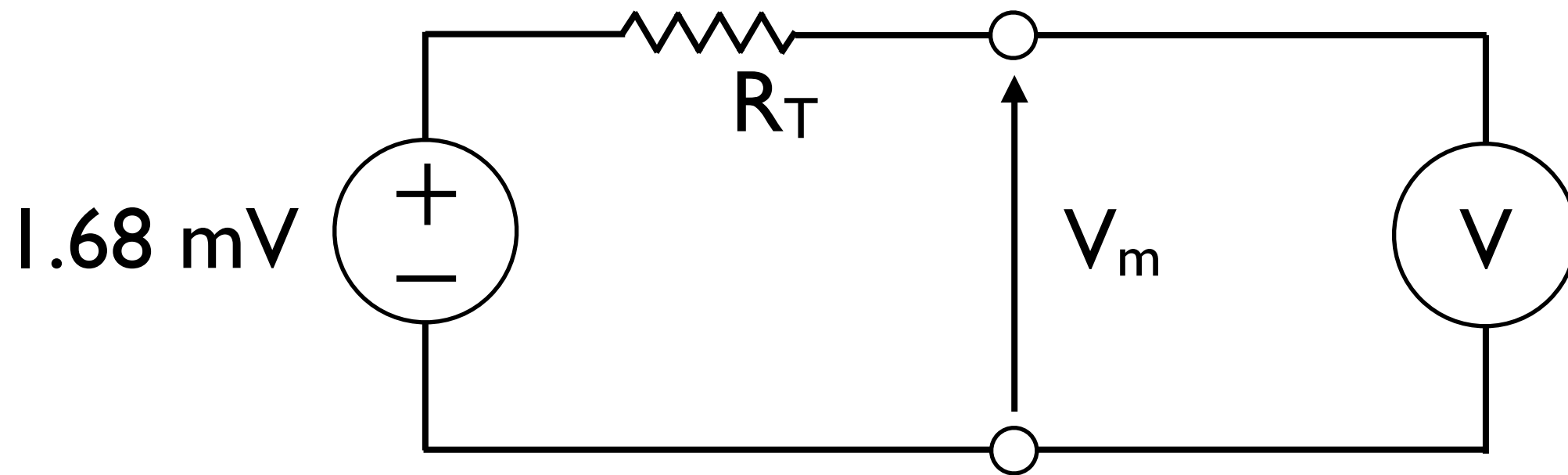
Problem n. 1: we **MUST** amplify the voltage



$$V_m = 1.68 \text{ mV} \cdot \frac{R_V}{R_V + R_T}$$


Problem n. 2: we must increase R_V as much as possible

OPERATIONAL AMPLIFIER

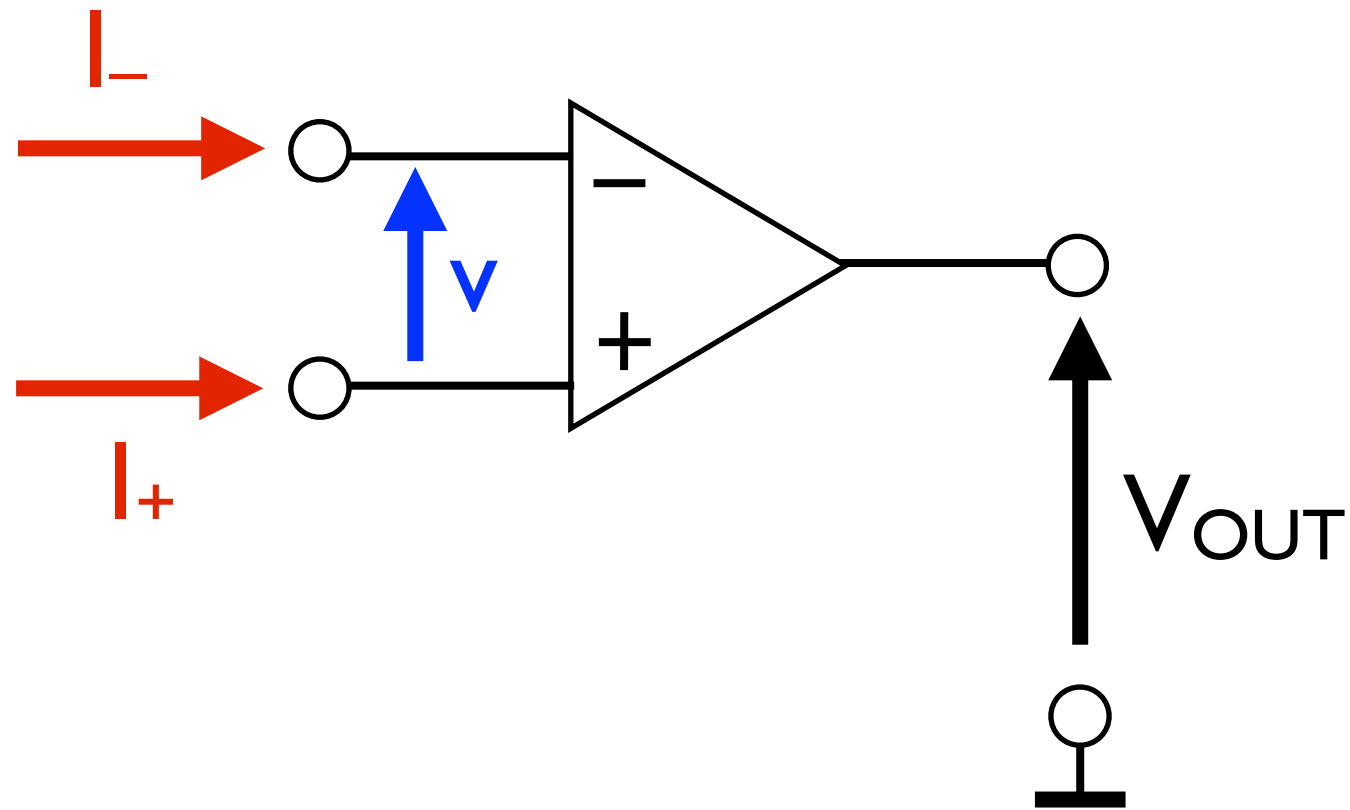


The opamp set the output voltage V_{OUT} to a value which assures the following conditions are fulfilled

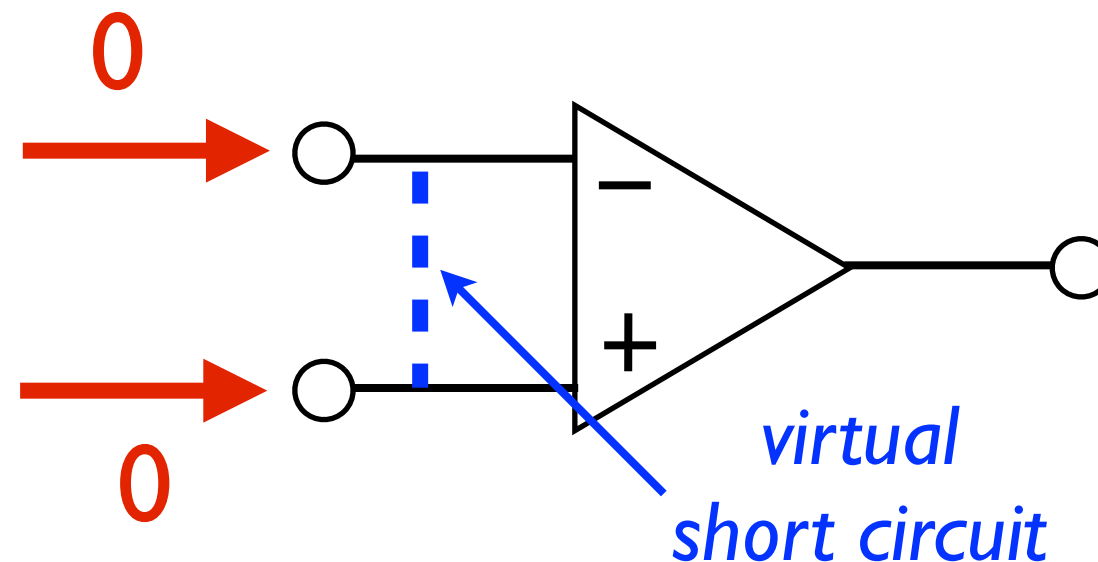- 1) $I_- = 0$
- 2) $I_+ = 0$
- 3) $v = 0$




INVERTING AMPLIFIER

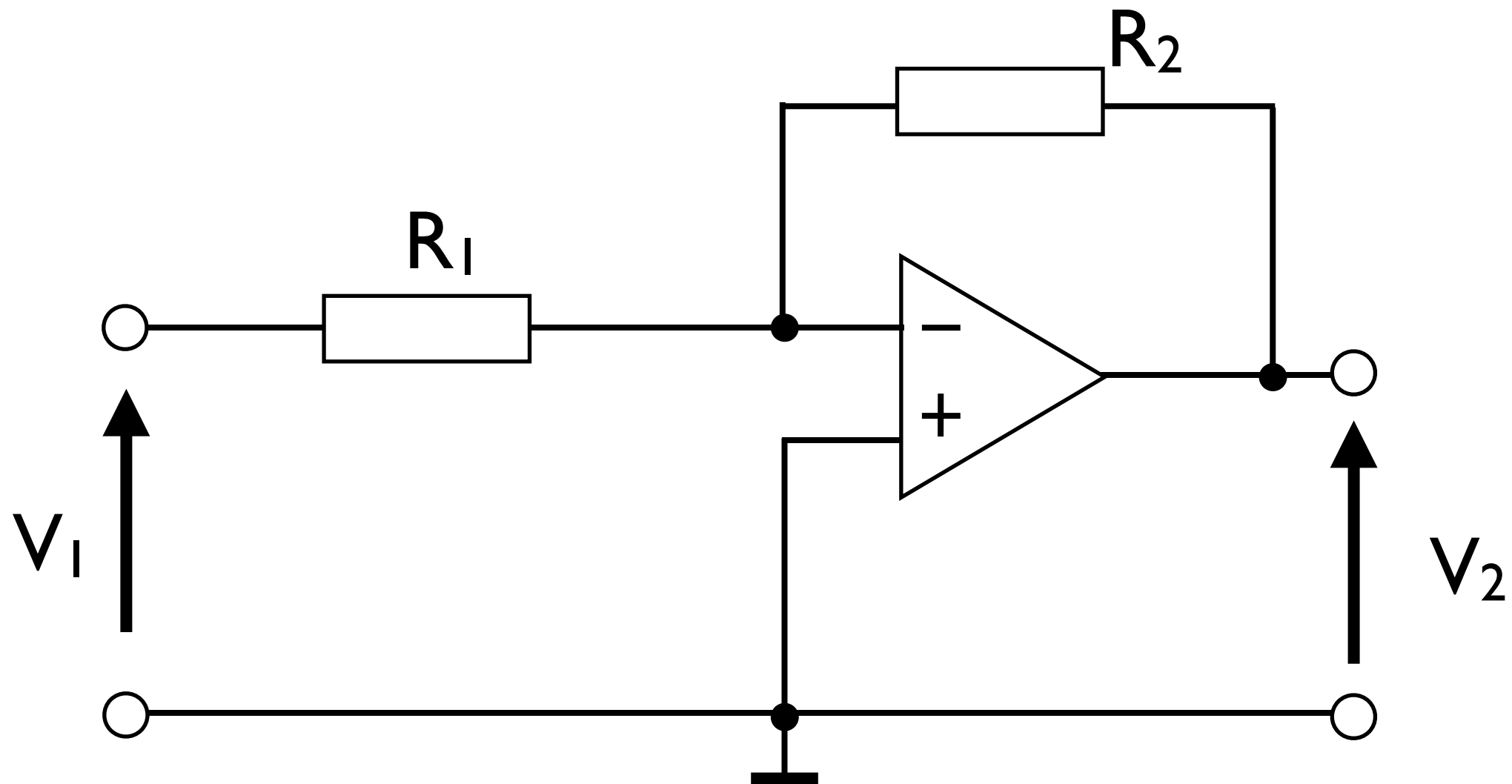

$$V_2 = -V_1 \cdot \frac{R_2}{R_1}$$


INVERTING AMPLIFIER

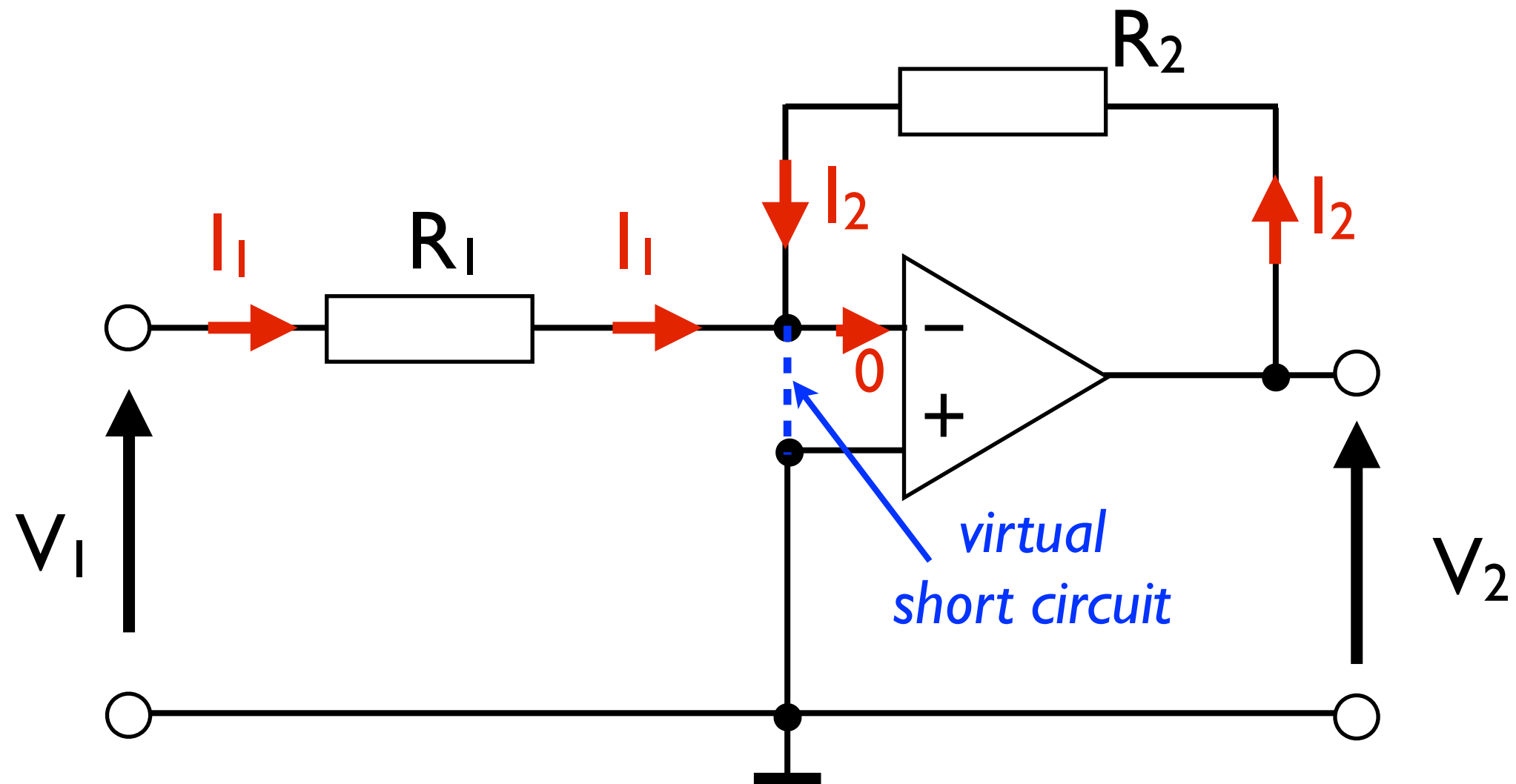

1) $I_1 = V_1 / R_1$



2) $V_2 = R_2 \cdot I_2$

3) $I_2 = -I_1$

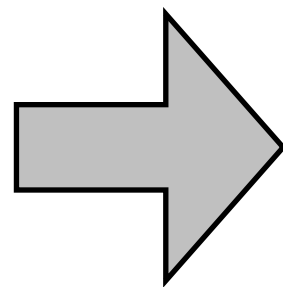


$$V_2 = -V_1 \cdot \frac{R_2}{R_1}$$

INVERTING AMPLIFIER

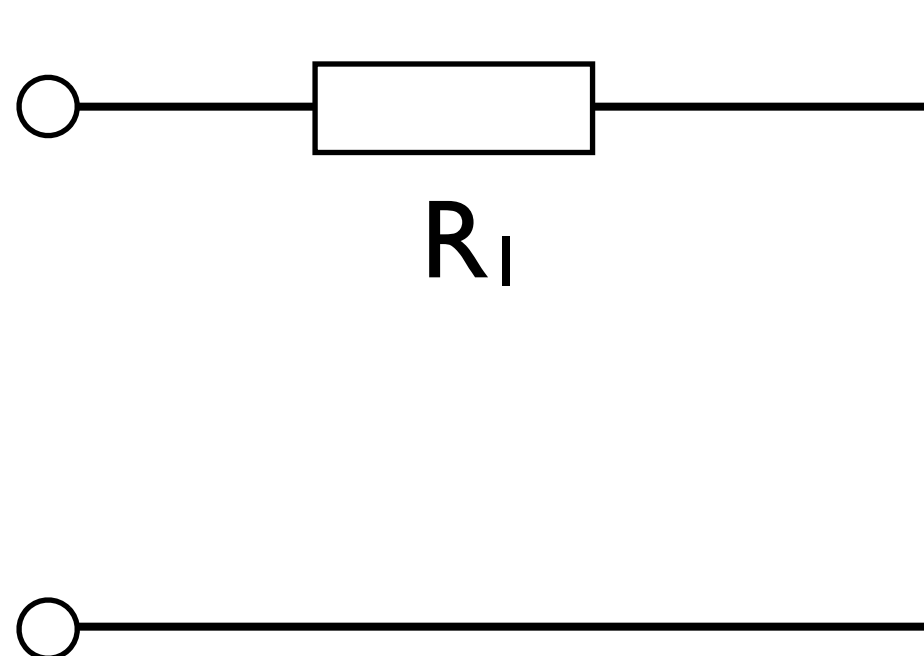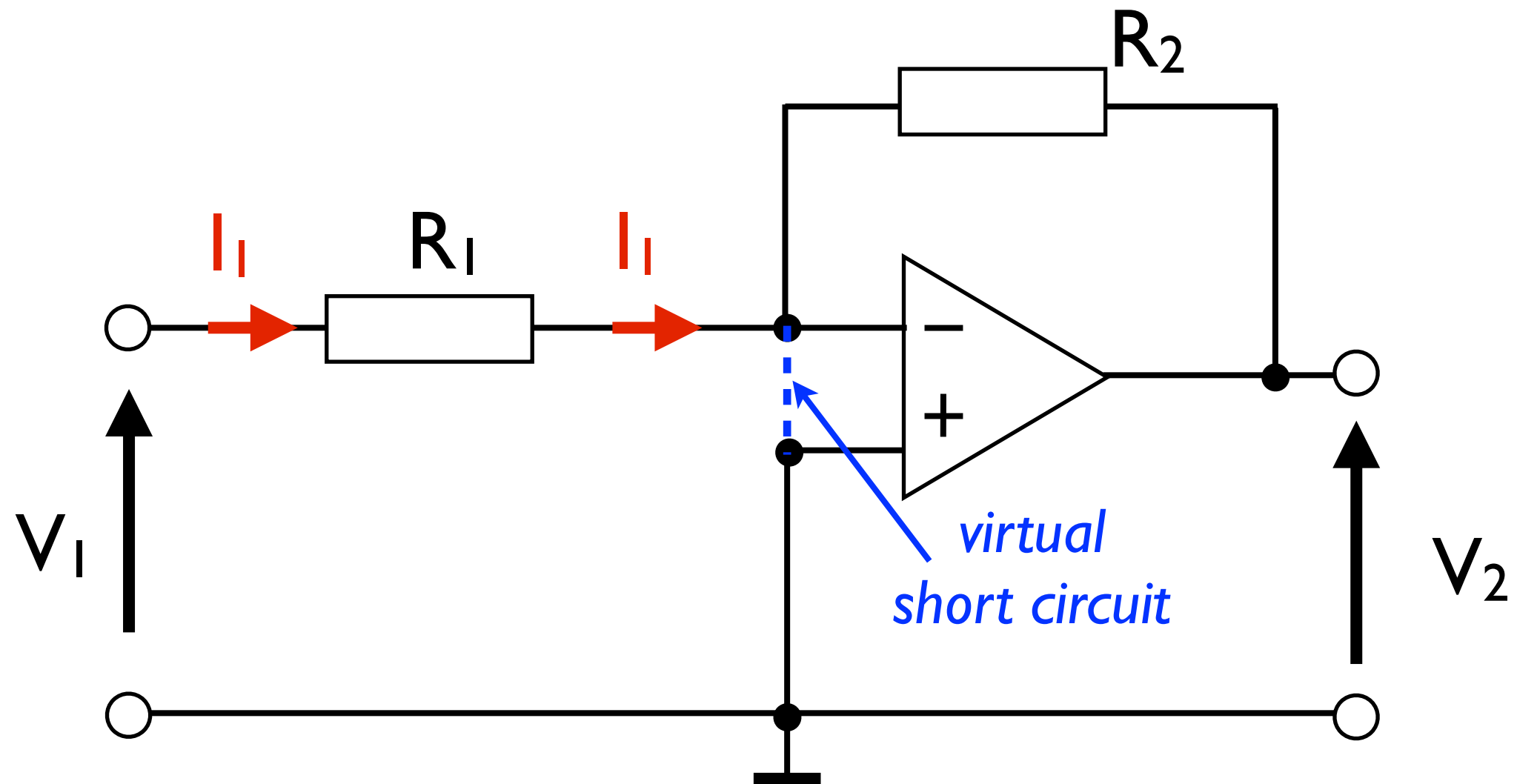


$$I_1 = V_1 / R_1$$

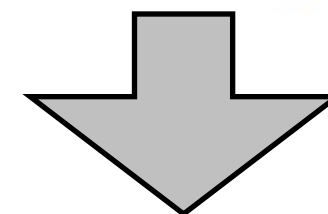


Input resistance R_1

NON-INVERTING AMPLIFIER

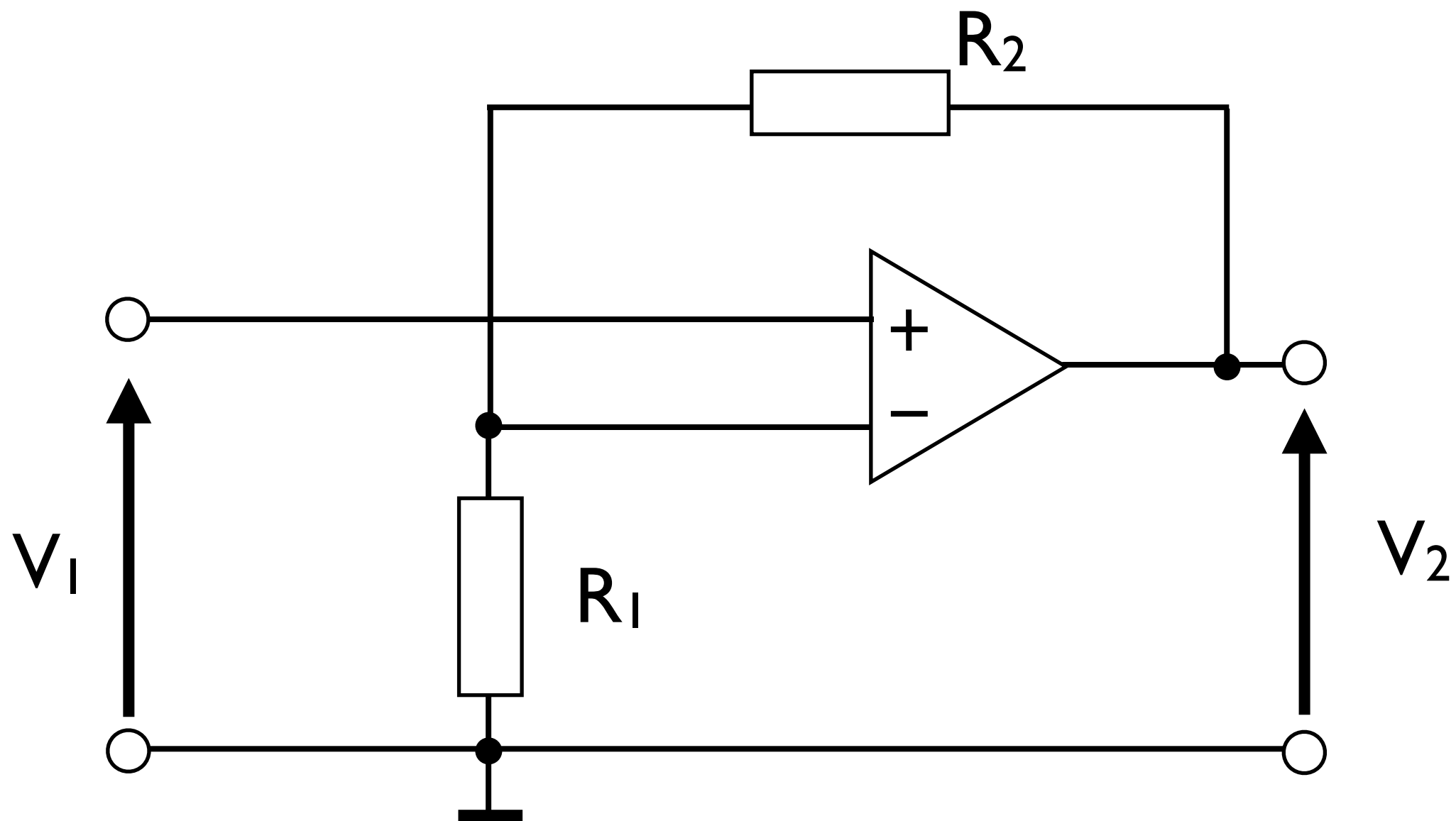

$$V_2 = \left(1 + \frac{R_2}{R_1} \right) \cdot V_1$$


NON-INVERTING AMPLIFIER

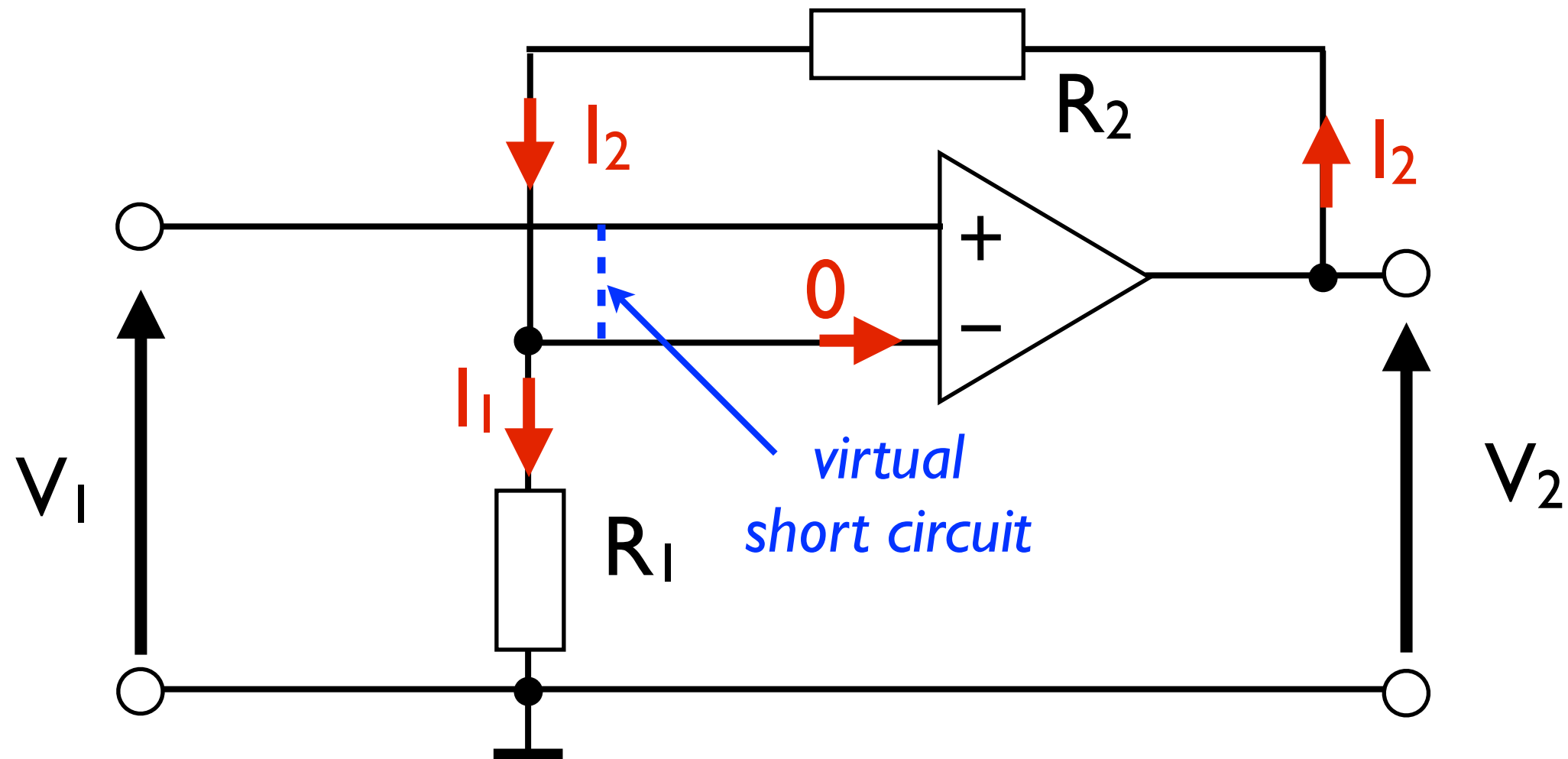

1) $I_1 = V_1 / R_1$




2) $I_2 = I_1$

3) $V_2 = R_2 \cdot I_2 + V_1$

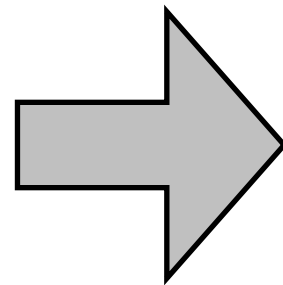


$$V_2 = \left(1 + \frac{R_2}{R_1} \right) \cdot V_1$$

NON-INVERTING AMPLIFIER

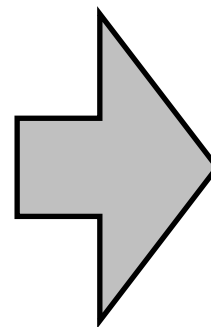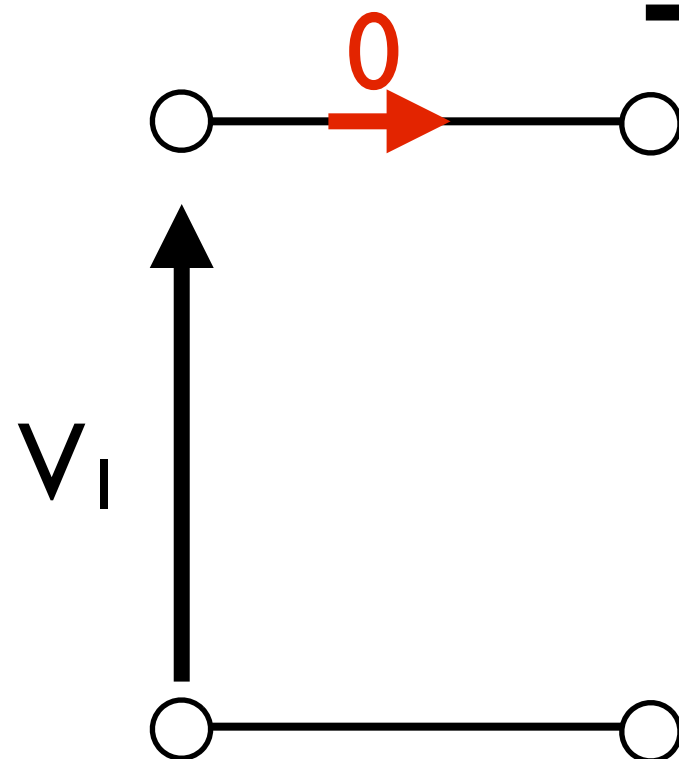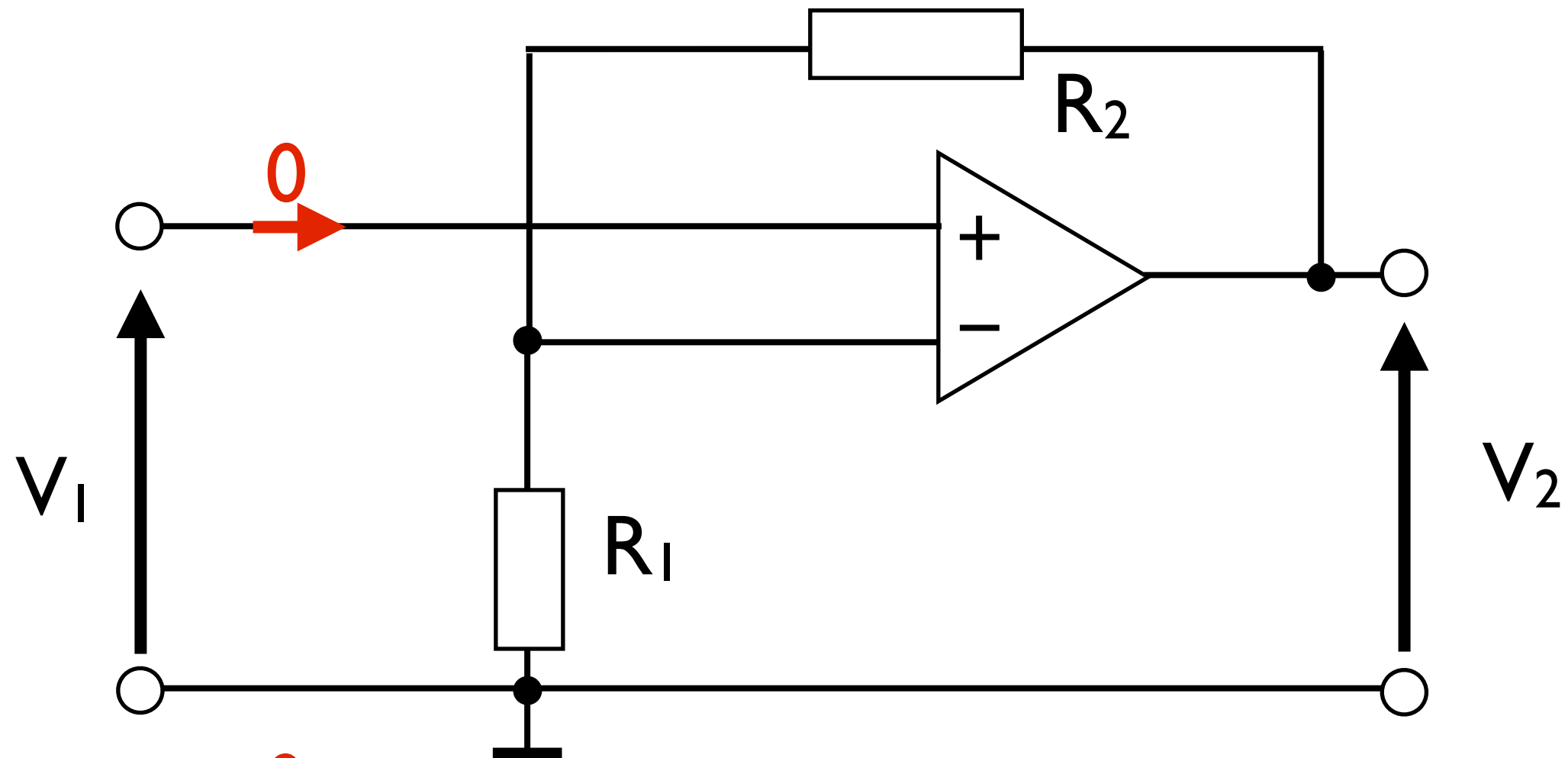


Input resistance ∞

VOLTAGE FOLLOWER

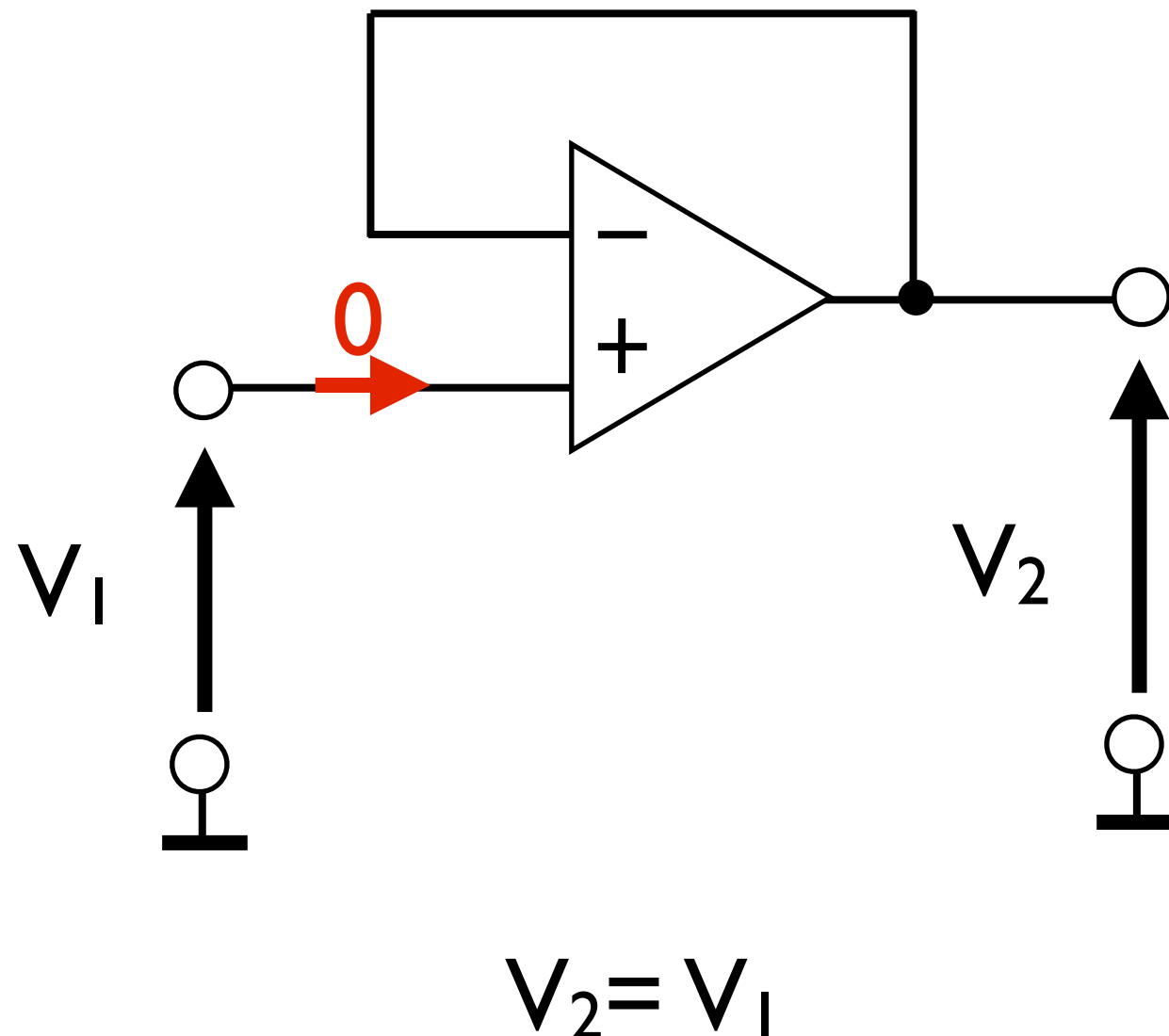


Input resistance ∞
Output resistance 0

IDEAL OPAMP

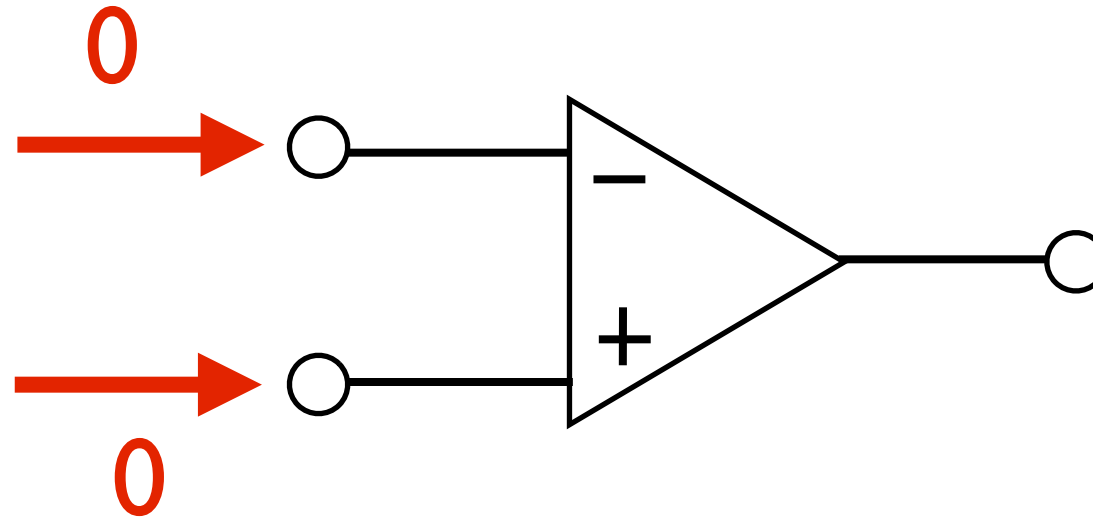


REAL OPAMP

I) Bias currents

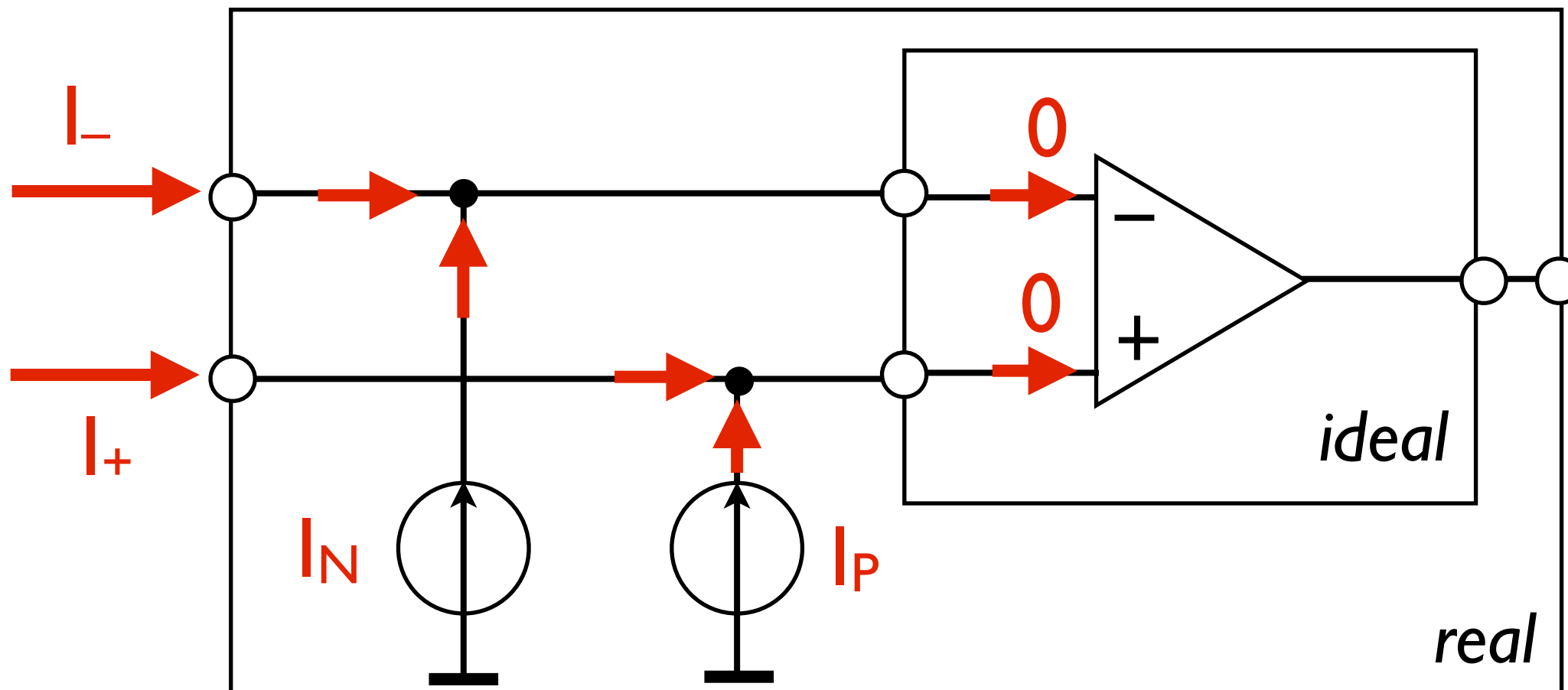


IDEAL OPAMP

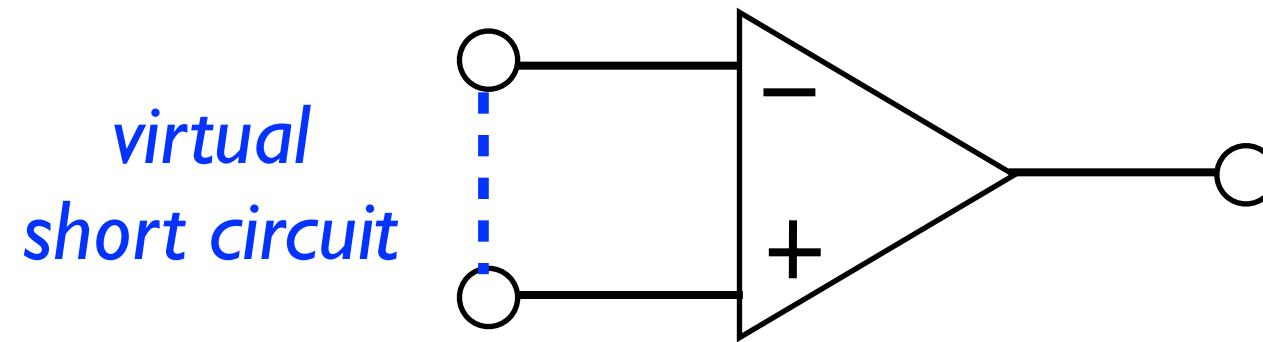


REAL OPAMP

2) offset voltage

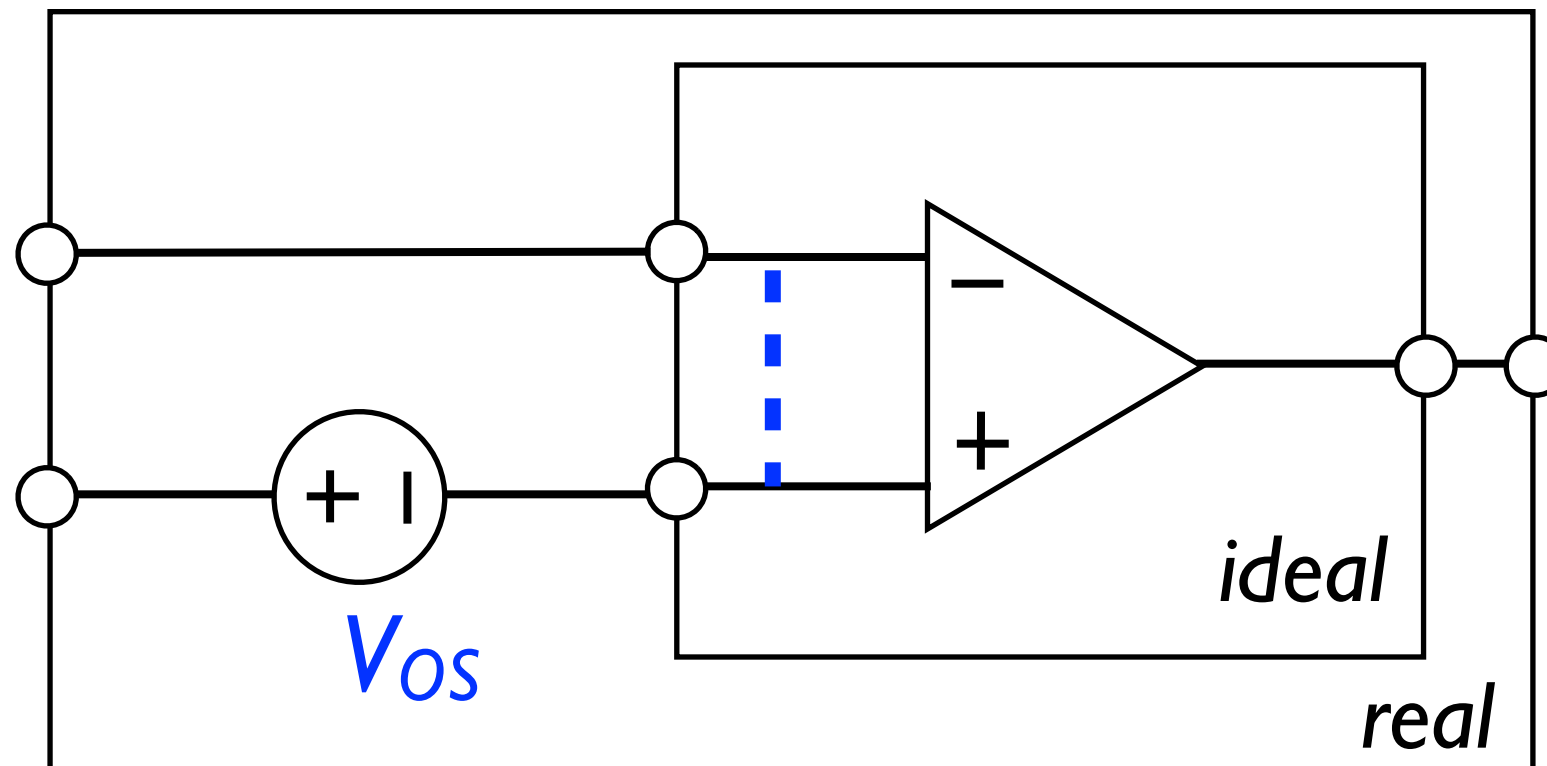


REAL INVERTING AMPLIFIER

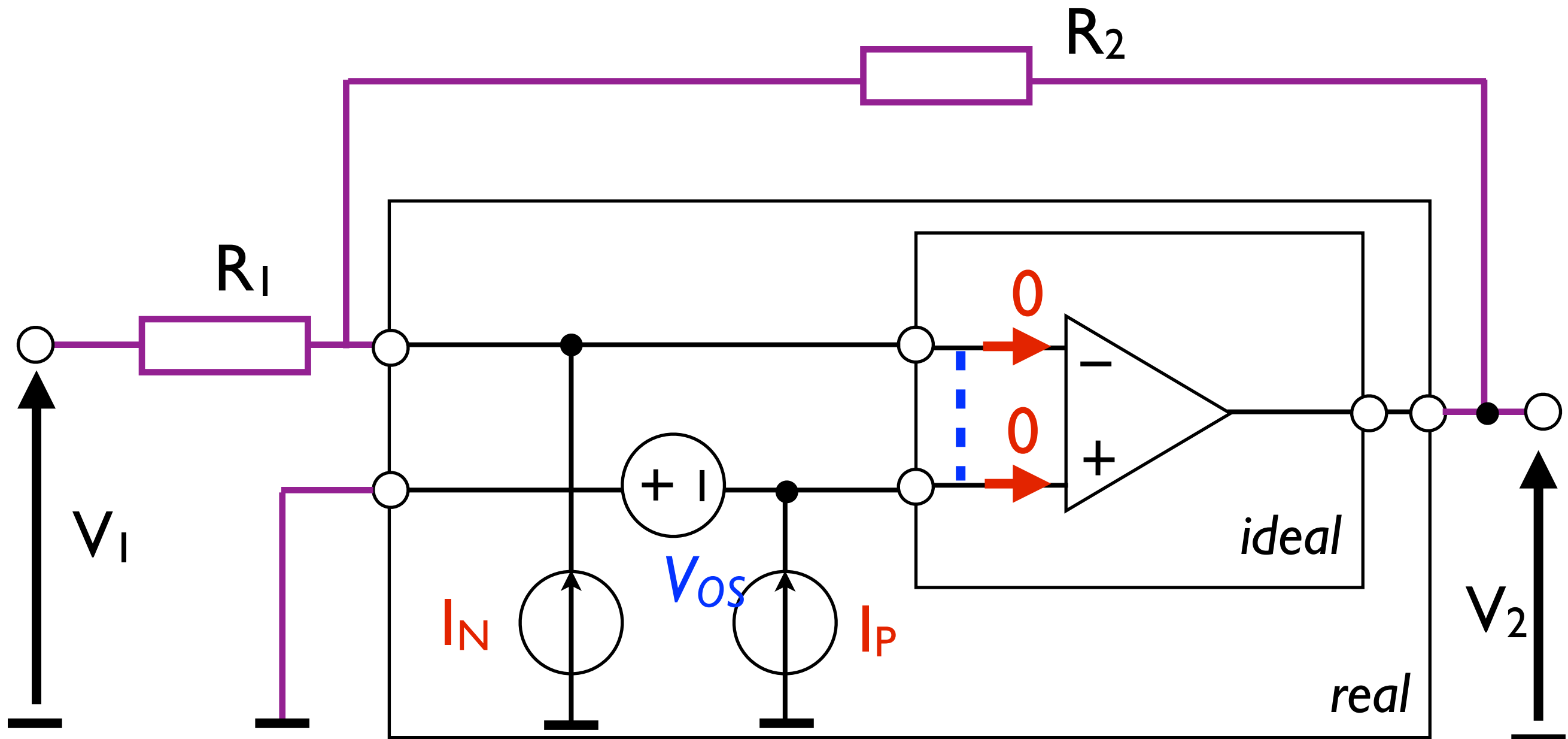

REAL INVERTING AMPLIFIER

- effect of I_P

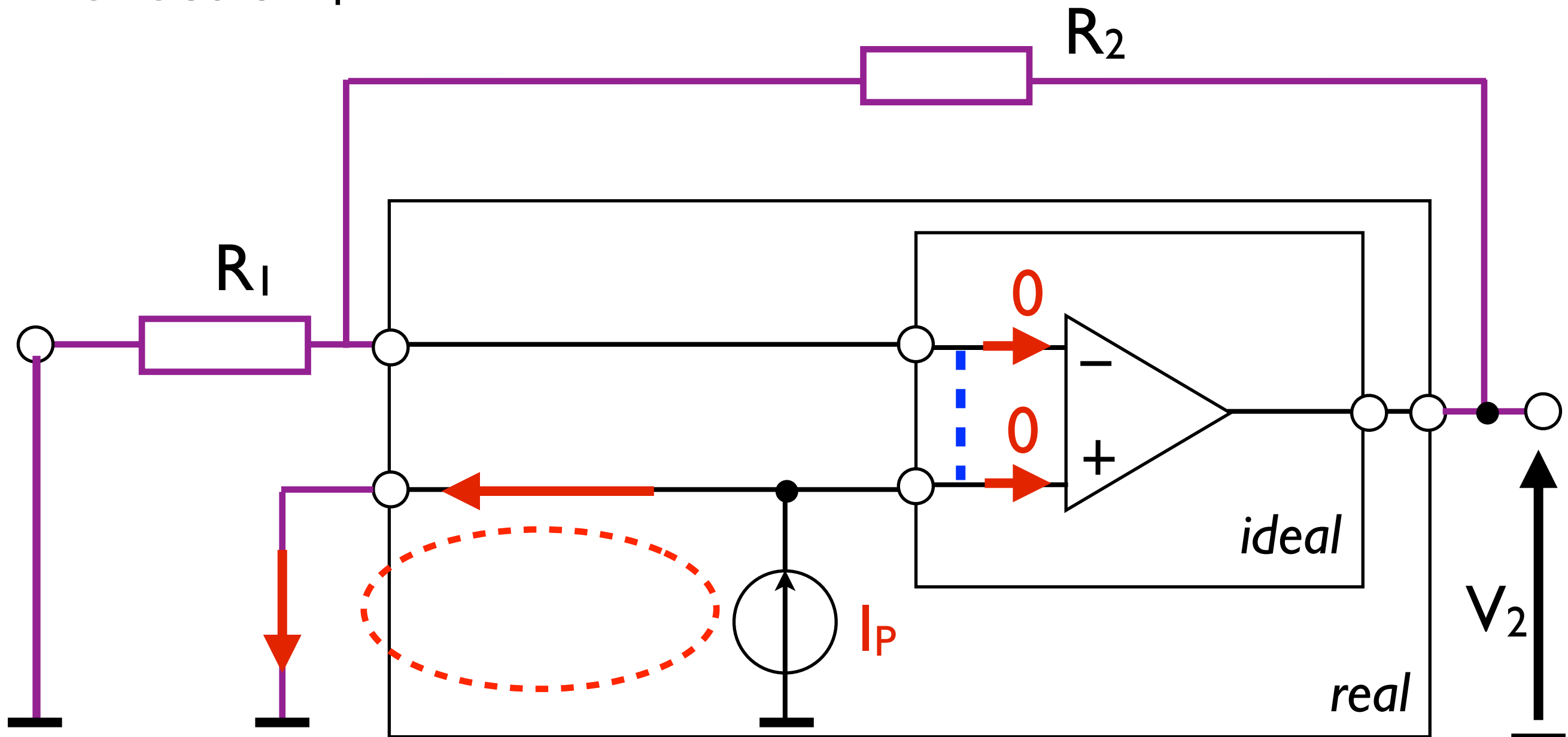


$$V_2=0$$

I_P has no effect on V_2

REAL INVERTING AMPLIFIER

- effect of I_N

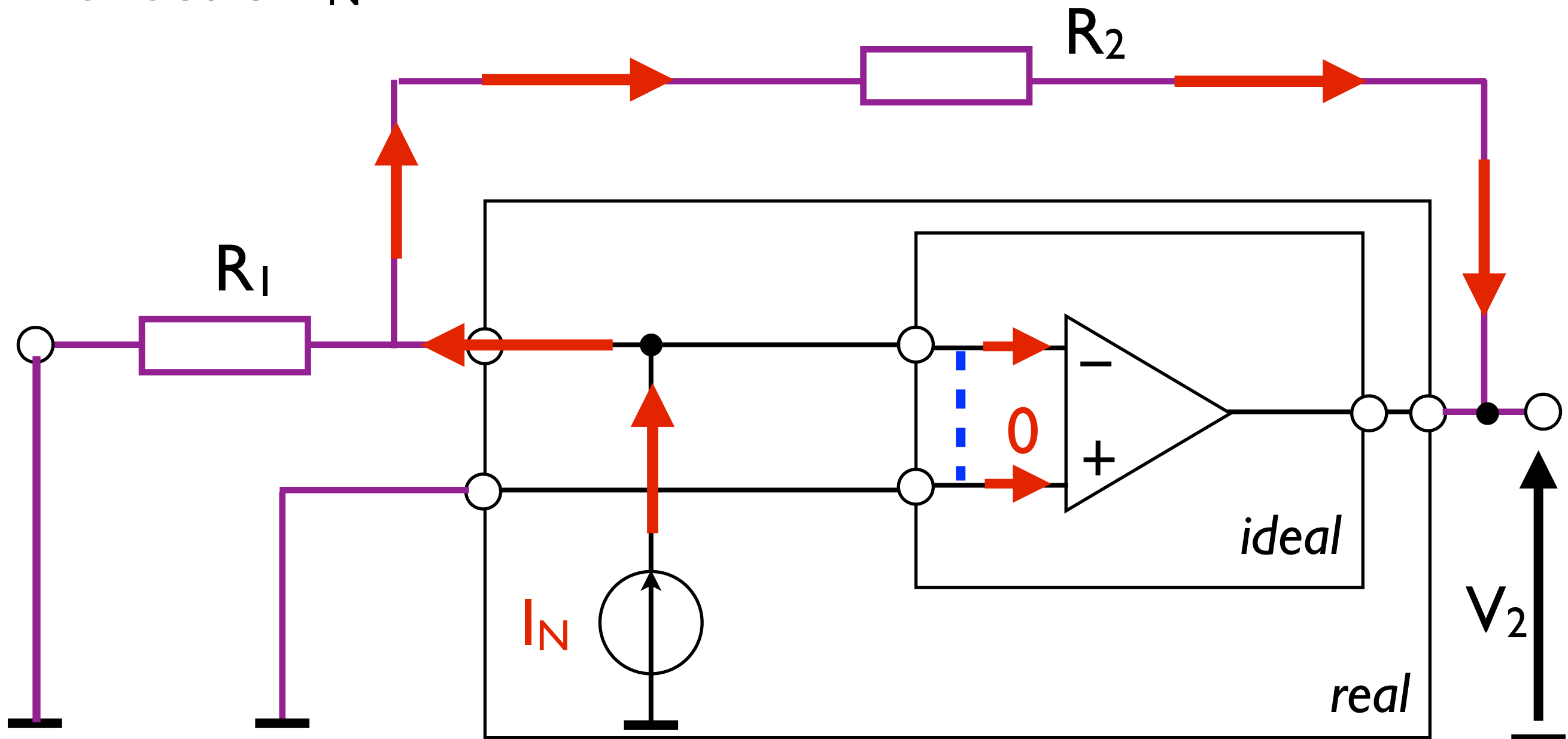


The current in R_1 is 0 because R_1 is short-circuited

$$V_2 = R_2 \cdot I_N$$

REAL INVERTING AMPLIFIER

- effect of V_{os}

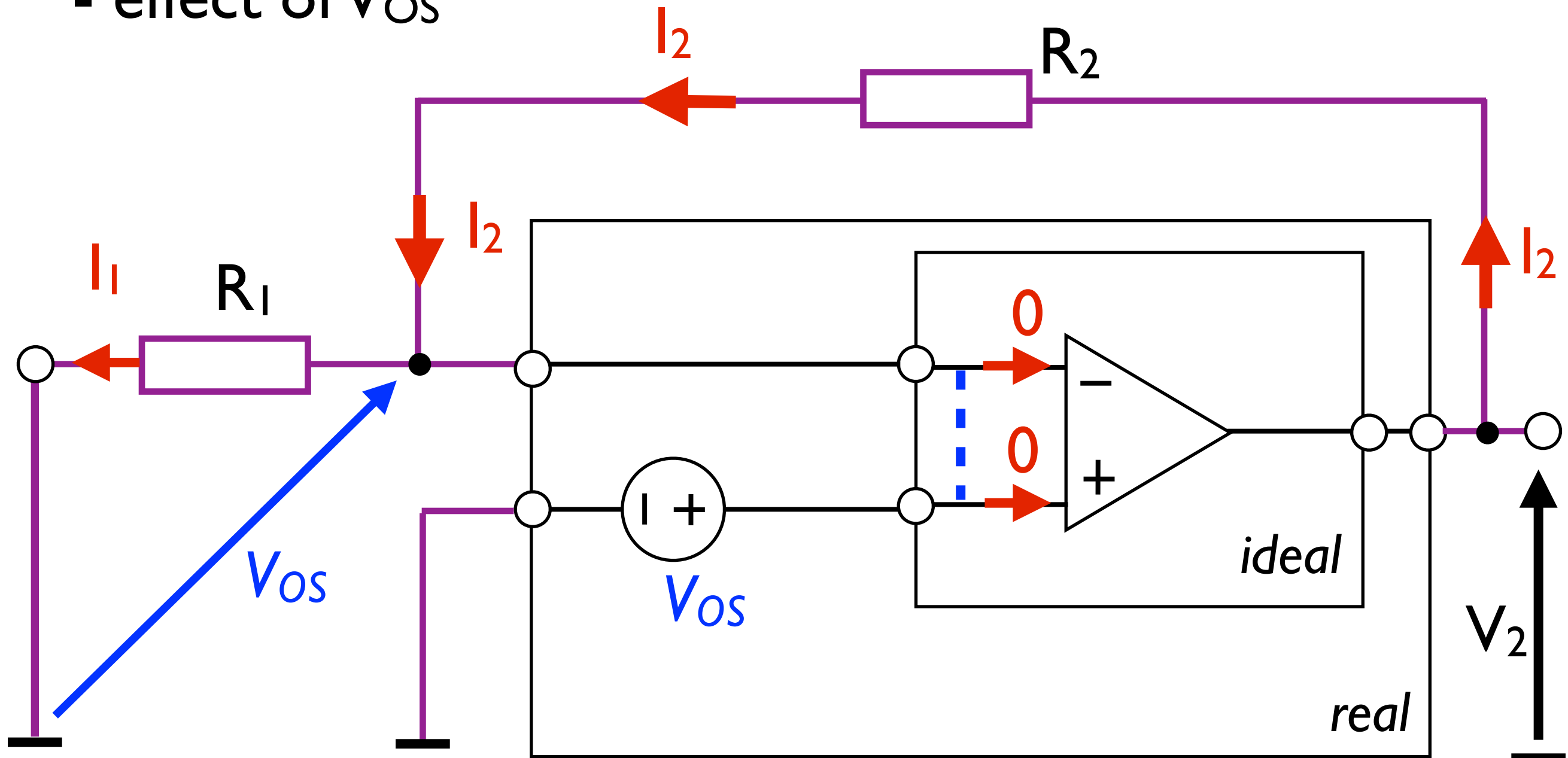

$$I_1 = V_{os} / R_1 \quad ; \quad I_2 = I_1 \quad ; \quad V_2 = \frac{V_{os}}{R_1} \cdot R_2 + V_{os}$$

REAL INVERTING AMPLIFIER

Taking all the contributions into account

$$V_2 = -\frac{R_2}{R_1} \cdot V_1 \pm R_2 \cdot I_N \pm V_{OS} \left(1 + \frac{R_2}{R_1} \right)$$

The input voltage will be recalculated as:

$$V_1 = -\frac{R_1}{R_2} \cdot V_2 \mp R_1 \cdot I_N \mp V_{OS} \left(1 + \frac{R_1}{R_2} \right)$$

UNCERTAINTY: IDEAL INVERTING AMPLIFIER


$$V_1 = -\frac{R_1}{R_2} \cdot V_2$$

derivates to all variables

$$\frac{dV_1}{dV_2} = -\frac{R_1}{R_2}$$

$$\frac{dV_1}{dR_1} = -\frac{V_2}{R_2}$$

$$\frac{dV_1}{dR_2} = \frac{R_1}{R_2^2} \cdot V_2$$

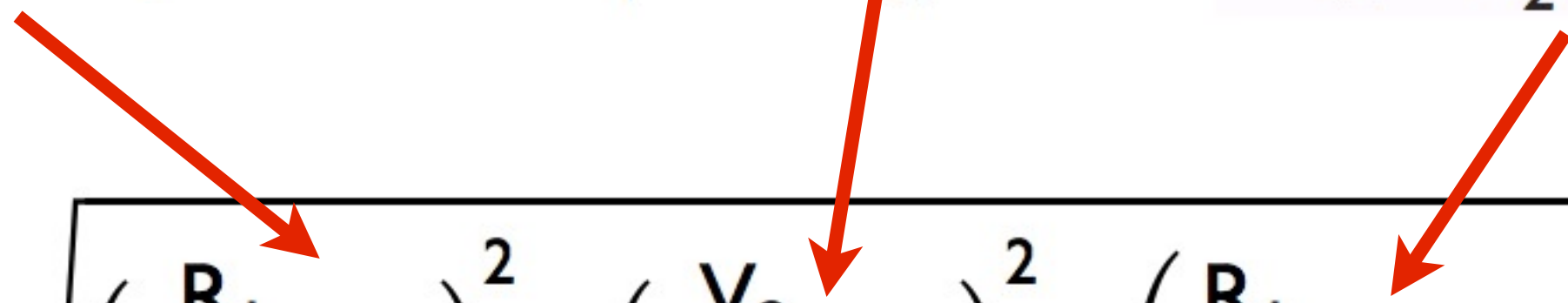
$$u_{V_1}|_{id} = \sqrt{\left(-\frac{R_1}{R_2} \cdot u_{V_2}\right)^2 + \left(-\frac{V_2}{R_2} \cdot u_{R_1}\right)^2 + \left(\frac{R_1}{R_2^2} \cdot V_2 \cdot u_{R_2}\right)^2}$$

UNCERTAINTY: **REAL** INVERTING AMPLIFIER


$$V_1 = -\frac{R_1}{R_2} \cdot V_2 \mp R_1 \cdot \mathbf{I_N} \mp \mathbf{V_{Os}} \left(1 + \frac{R_1}{R_2} \right)$$

ideal

additional sources of uncertainty


$$u_{V_1}|_{\text{real}} = \sqrt{u_{V_1}|_{\text{id}}^2 \mp \left(\frac{R_1 \cdot \mathbf{I_N}}{\sqrt{3}} \right)^2 \mp \left(\frac{\mathbf{V_{Os}} \left(1 + \frac{R_1}{R_2} \right)}{\sqrt{3}} \right)^2}$$

REAL NON-INVERTING AMPLIFIER

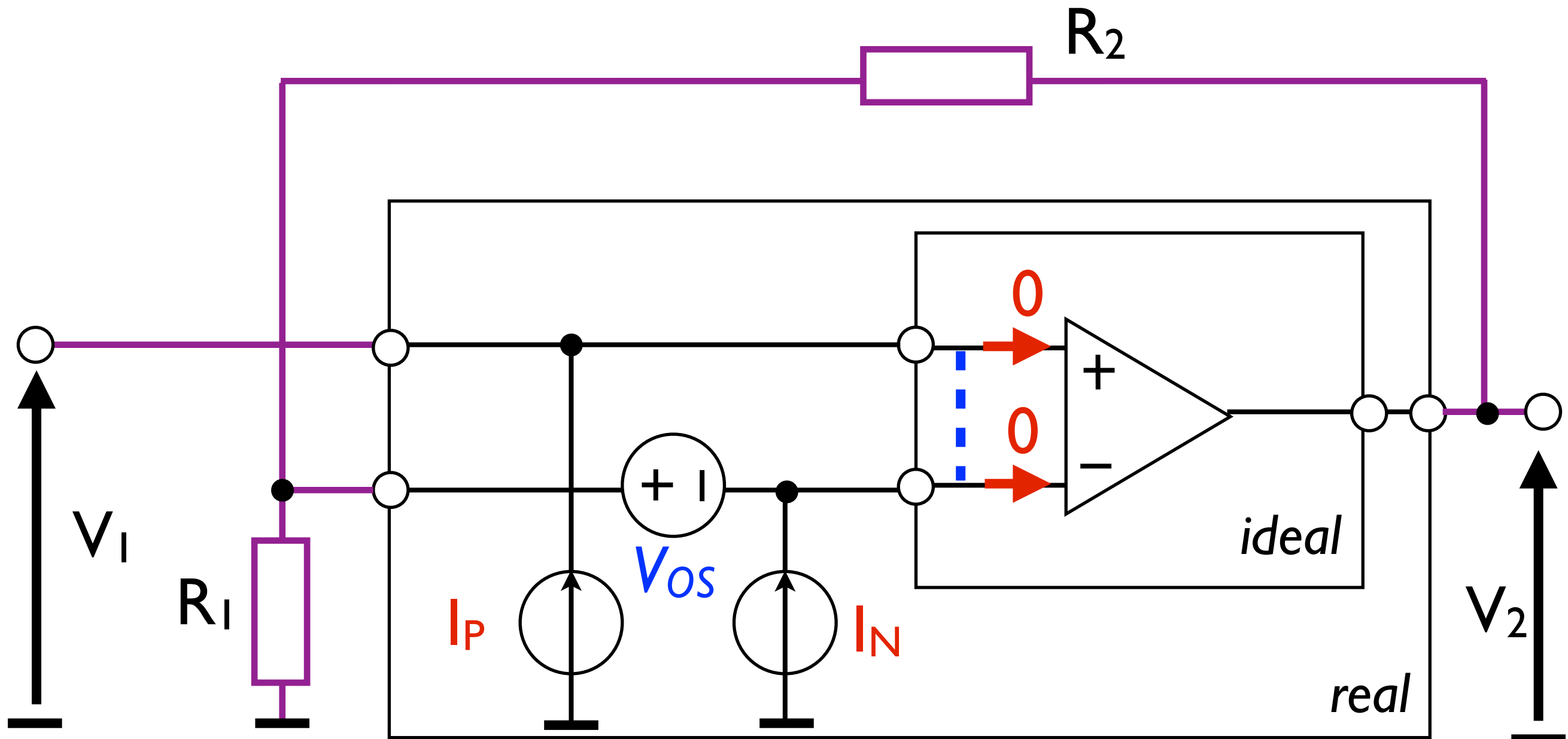

REAL NON-INVERTING AMPLIFIER

- effect of I_P

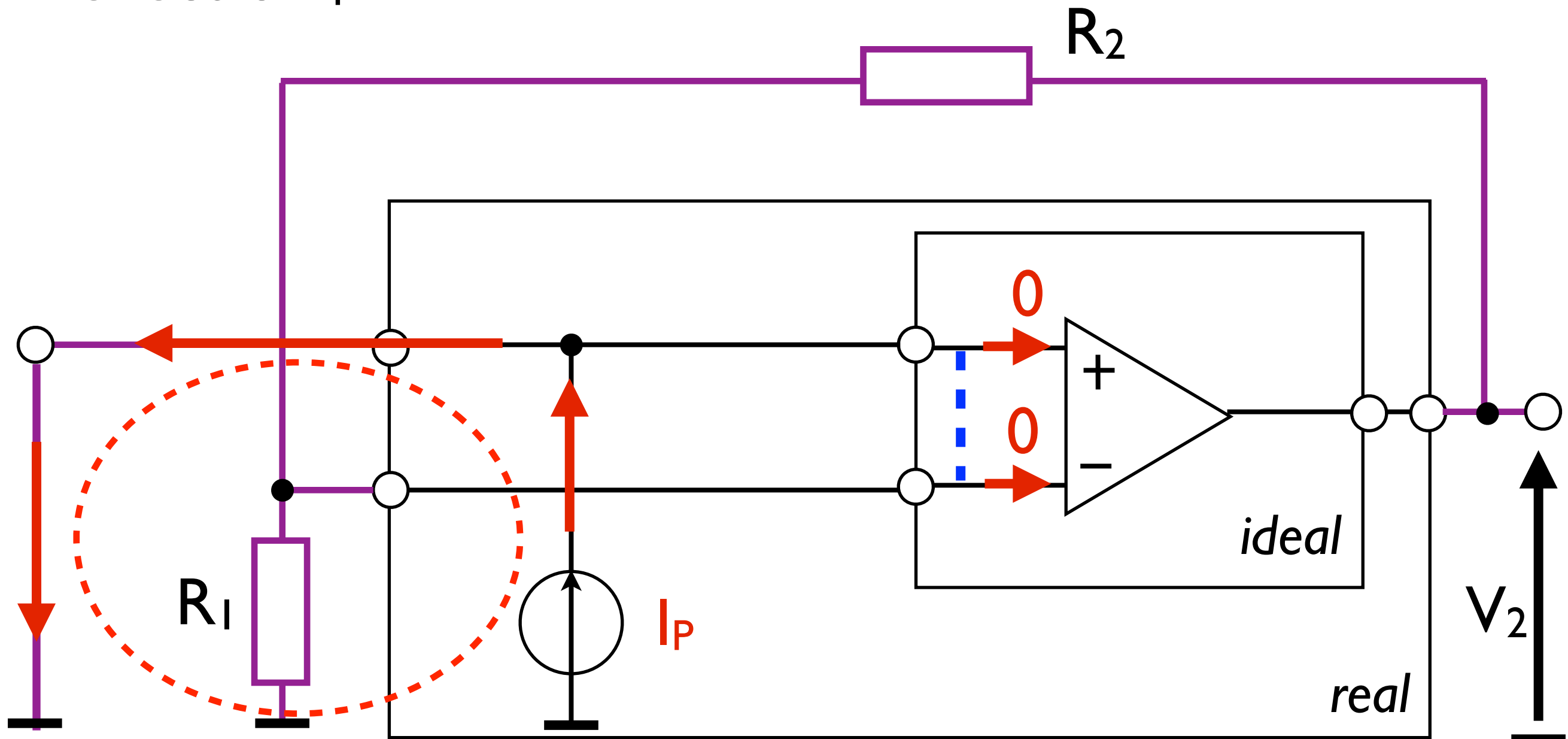


I_P has no effect on V_2

$$V_2 = 0$$

REAL NON-INVERTING AMPLIFIER

- effect of I_N

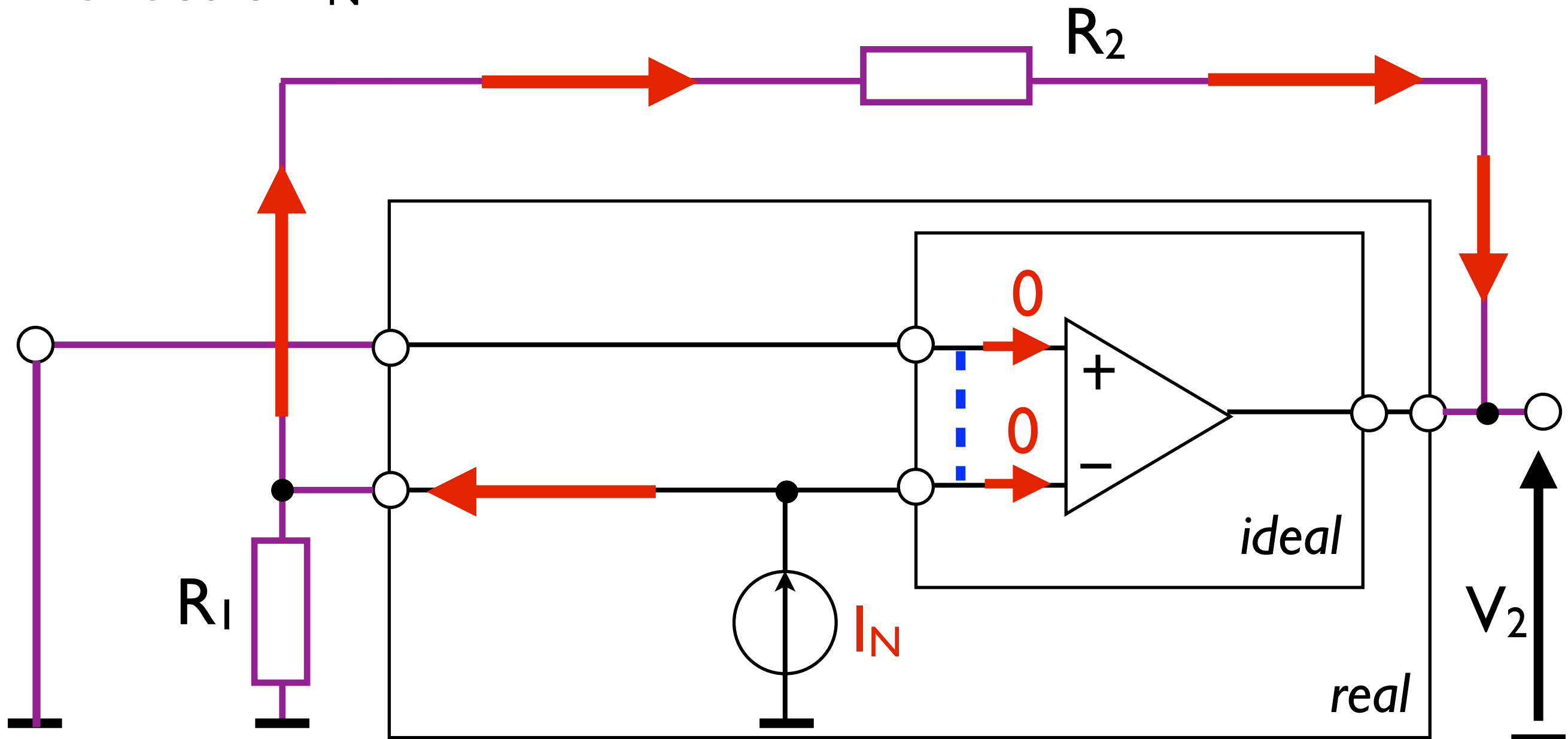


The current in R_1 is 0 because R_1 is short-circuited

$$V_2 = R_2 \cdot I_N$$

REAL NON-INVERTING AMPLIFIER

- effect of V_{os}

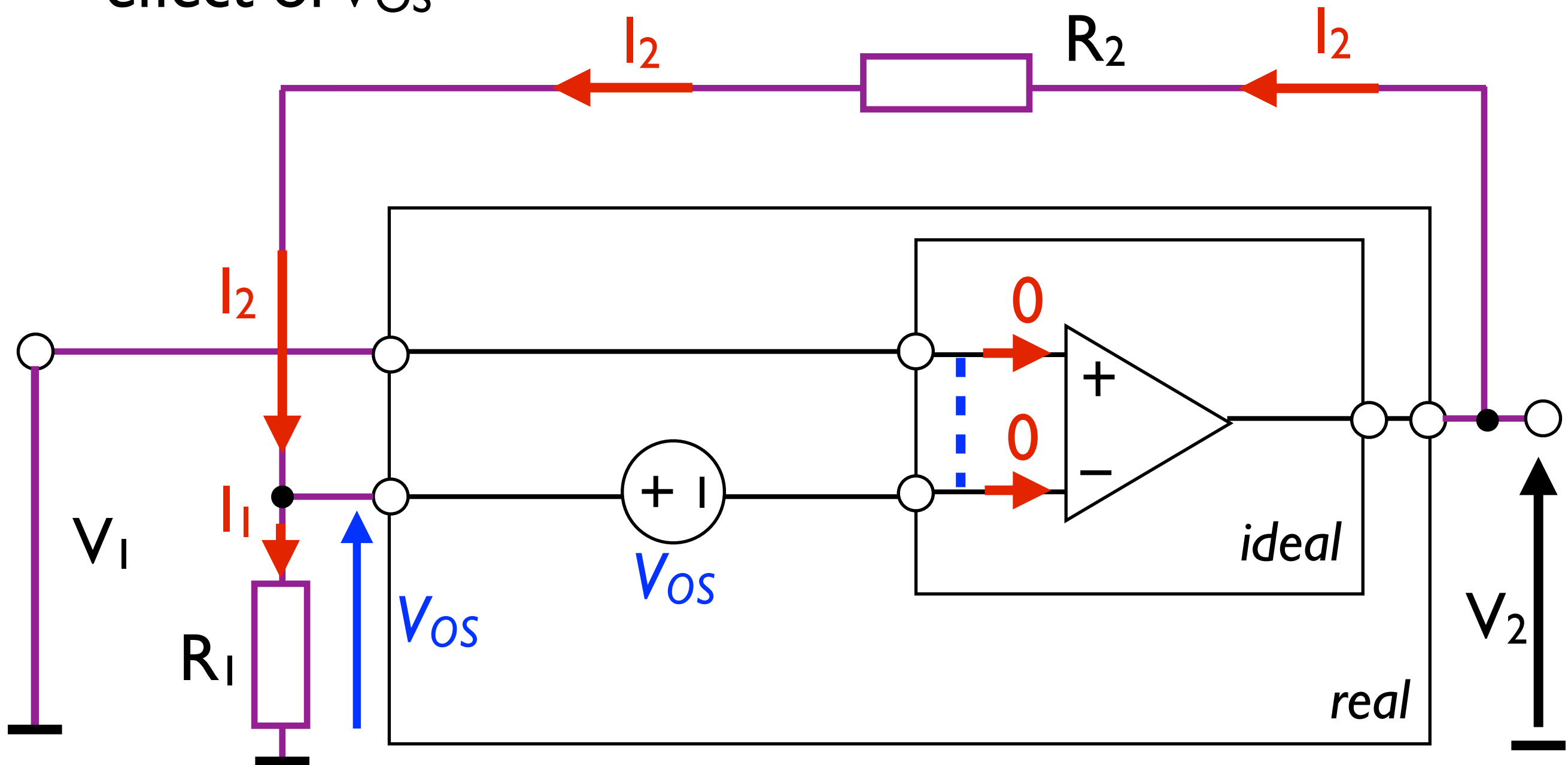

$$V_2 = \left(1 + \frac{R_2}{R_1} \right) V_{os}$$

REAL NON-INVERTING AMPLIFIER



Taking all the contributions into account

$$V_2 = \left(1 + \frac{R_2}{R_1}\right) V_1 \pm I_N \cdot R_2 \pm \left(1 + \frac{R_2}{R_1}\right) V_{OS}$$

The input voltage will be recalculated as:


$$V_1 = \left(\frac{R_1}{R_1 + R_2}\right) V_2 \mp I_N \cdot R_2 \left(\frac{R_1}{R_1 + R_2}\right) \mp V_{OS}$$

V_{os} can be nulled...

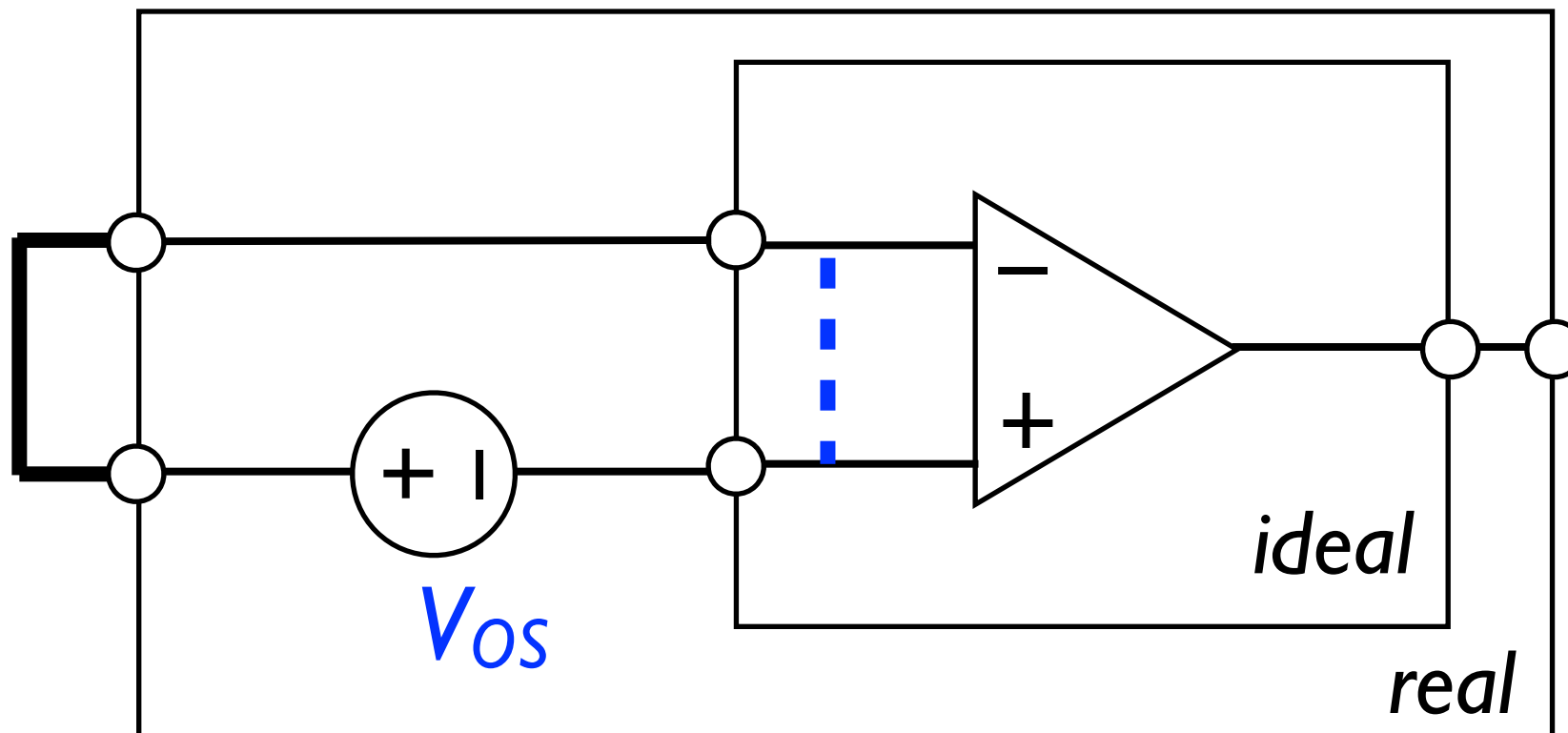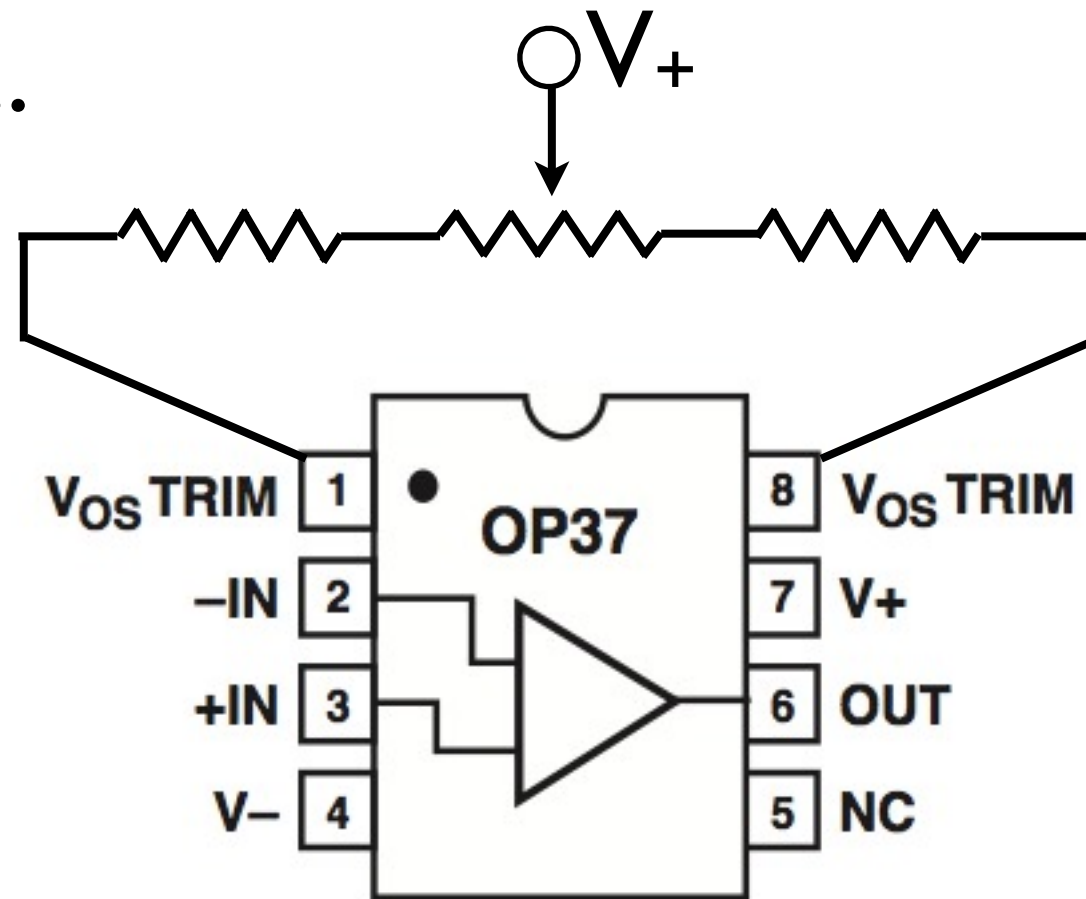


...but it drifts!

AUTOMATICALLY NULLED AMPLIFIER

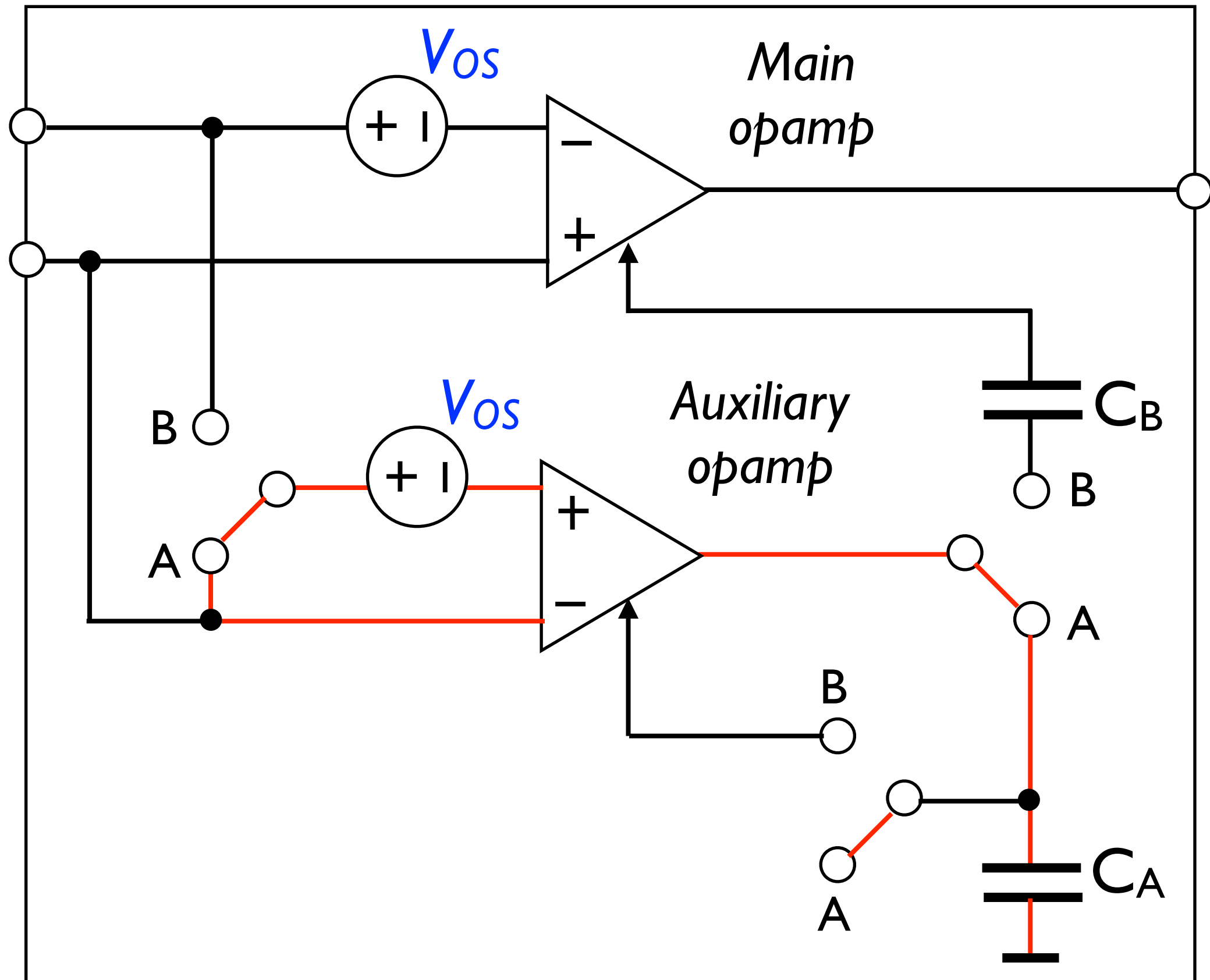


AUTOMATICALLY NULLED AMPLIFIER

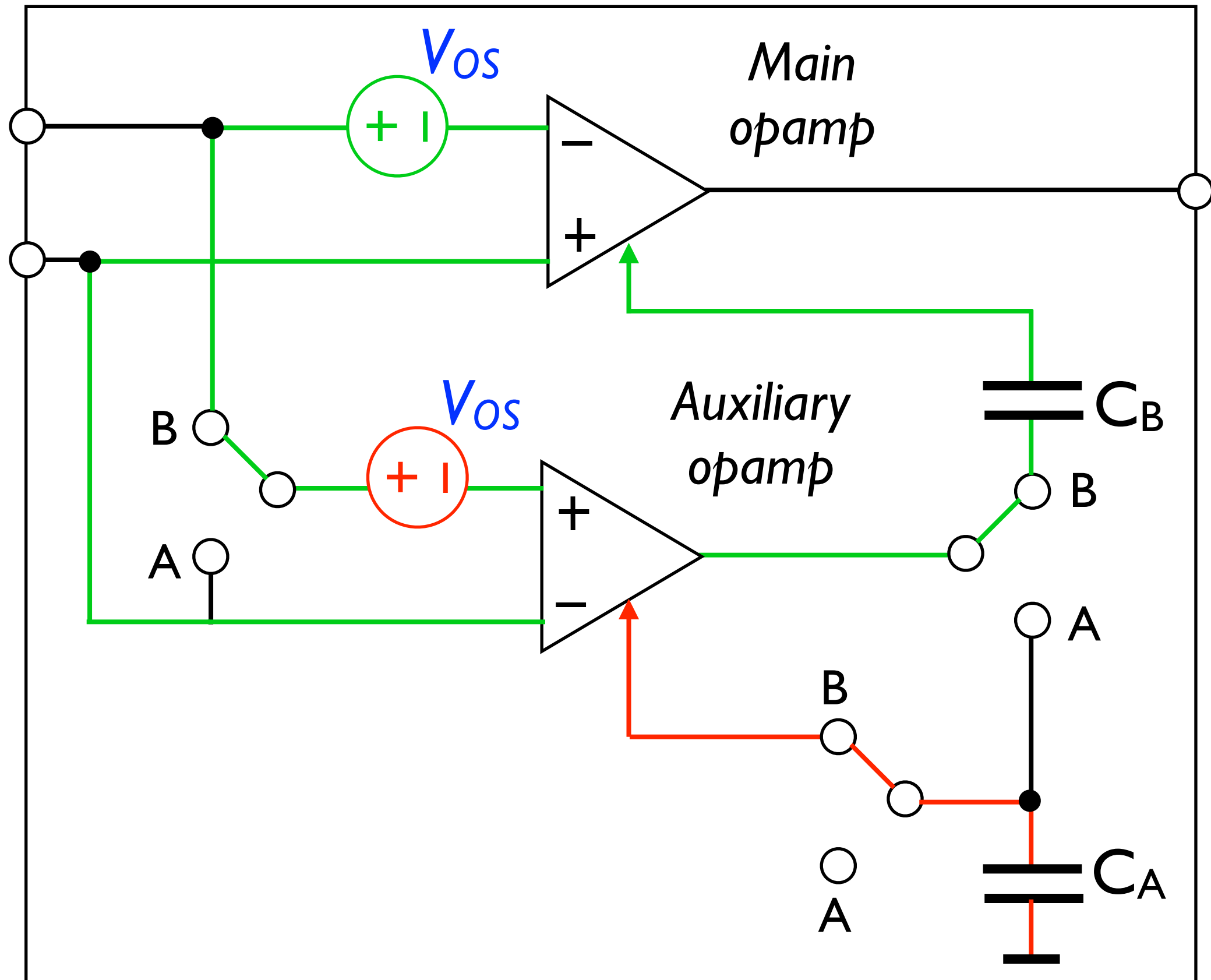

MEASUREMENT OF RESISTANCE

V-A method

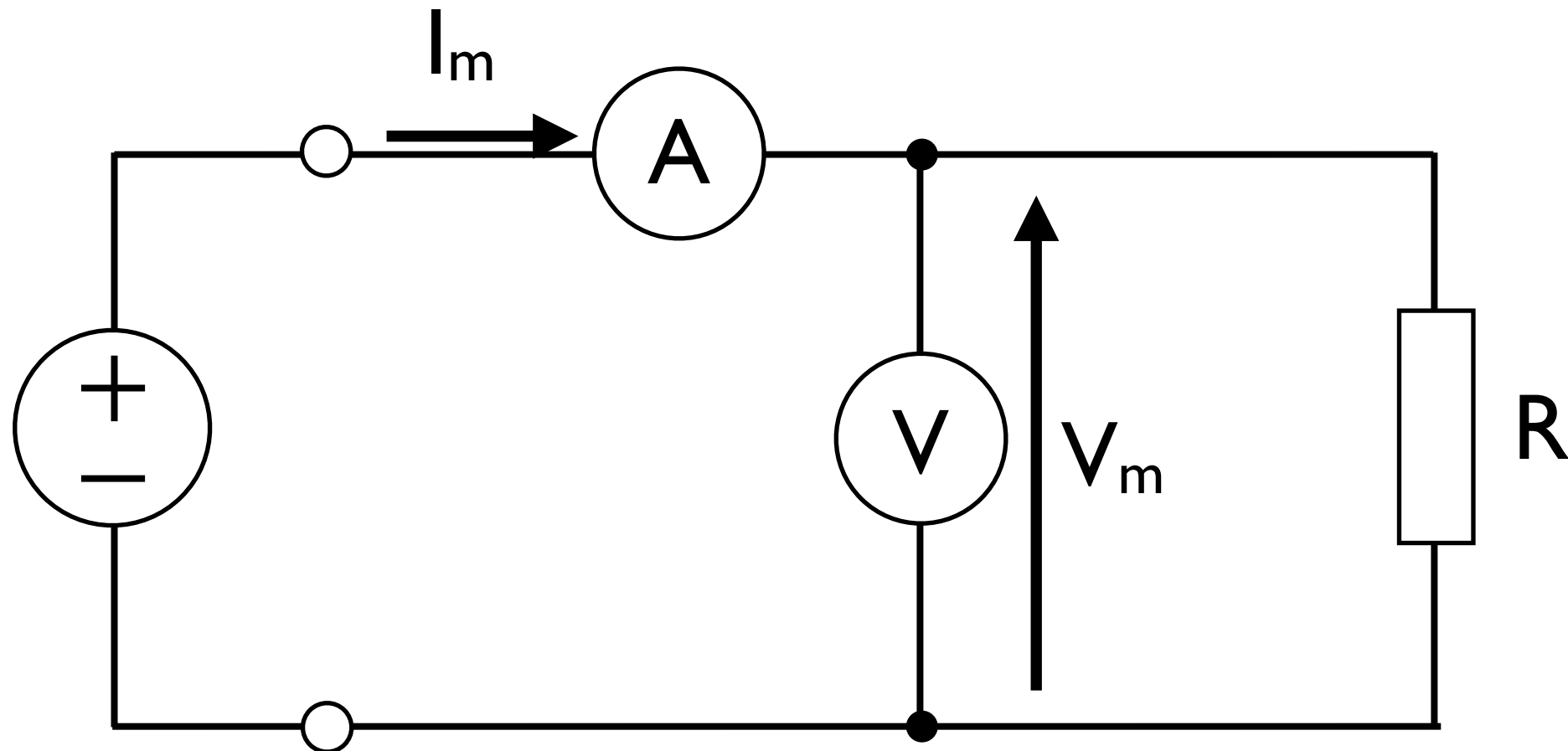(aka the simplest way to measure a resistance)



$$R = V_m / I_m$$

MEASUREMENT OF RESISTANCE

V-A method

Uncertainty

Function to derivate $R(V_m, I_m) = V_m / I_m$

Derivates: $\frac{dR}{dV_m} = \frac{1}{I_m}$

$$\frac{dR}{dI_m} = -\frac{V_m}{I_m^2}$$

Uncertainty of Resistance

$$\begin{aligned} u_R &= \sqrt{\left(\frac{dR}{dV_m} \cdot u_{V_m}\right)^2 + \left(\frac{dR}{dI_m} \cdot u_{I_m}\right)^2} \\ &= \sqrt{\left(\frac{1}{I_m} \cdot u_{V_m}\right)^2 + \left(-\frac{V_m}{I_m^2} \cdot u_{I_m}\right)^2} \end{aligned}$$


Let's check if units are correct:

$$u_R = \sqrt{\left(\frac{I}{I_m} \cdot u_{V_m}\right)^2 + \left(-\frac{V_m}{I_m^2} \cdot u_{I_m}\right)^2}$$


$$u_R = \sqrt{\left(\frac{I}{[A]} \cdot [V]\right)^2 + \left(-\frac{[V]}{[A]^2} \cdot [A]\right)^2}$$

$$u_R = \sqrt{([\Omega])^2 + ([\Omega])^2} = [\Omega]$$

Problem: non-ideal instruments

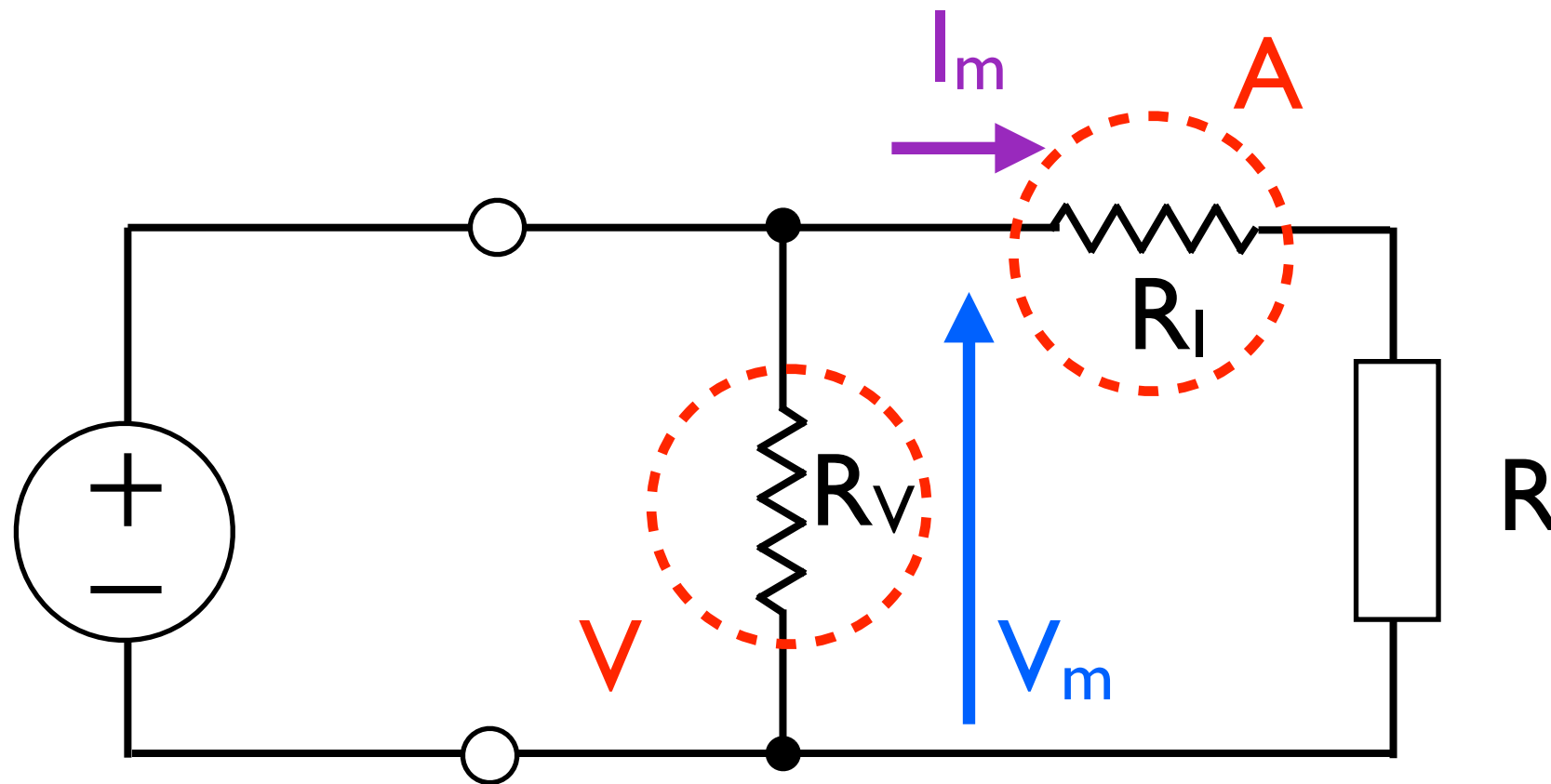

$$R_m = V_m / I_m = R_i + R$$


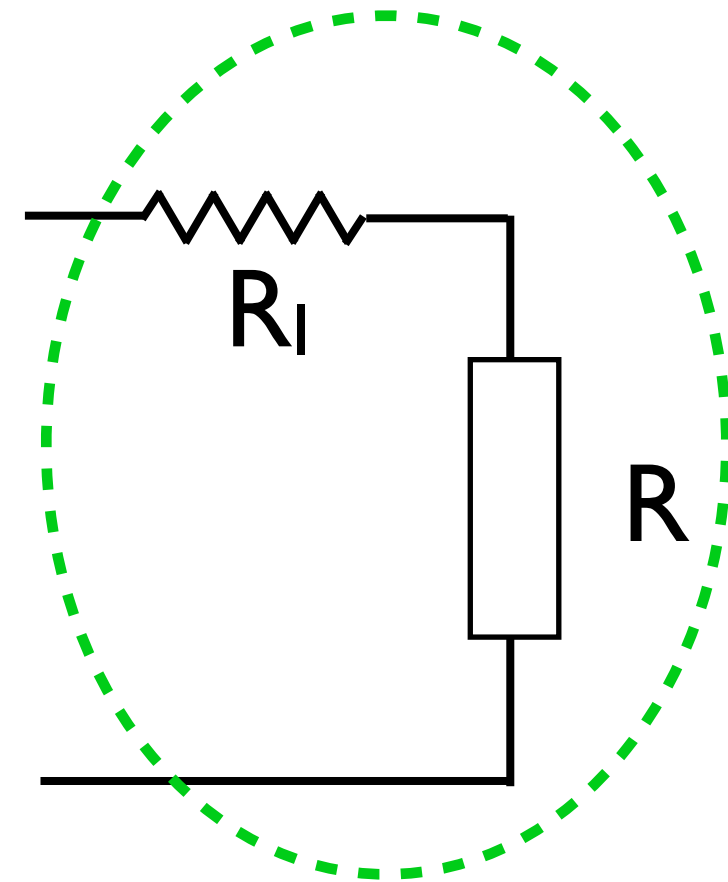


what you
measure

Correction of measured value

$$R = \frac{V_m}{I_m} - R_i$$

Problem: non-ideal instruments

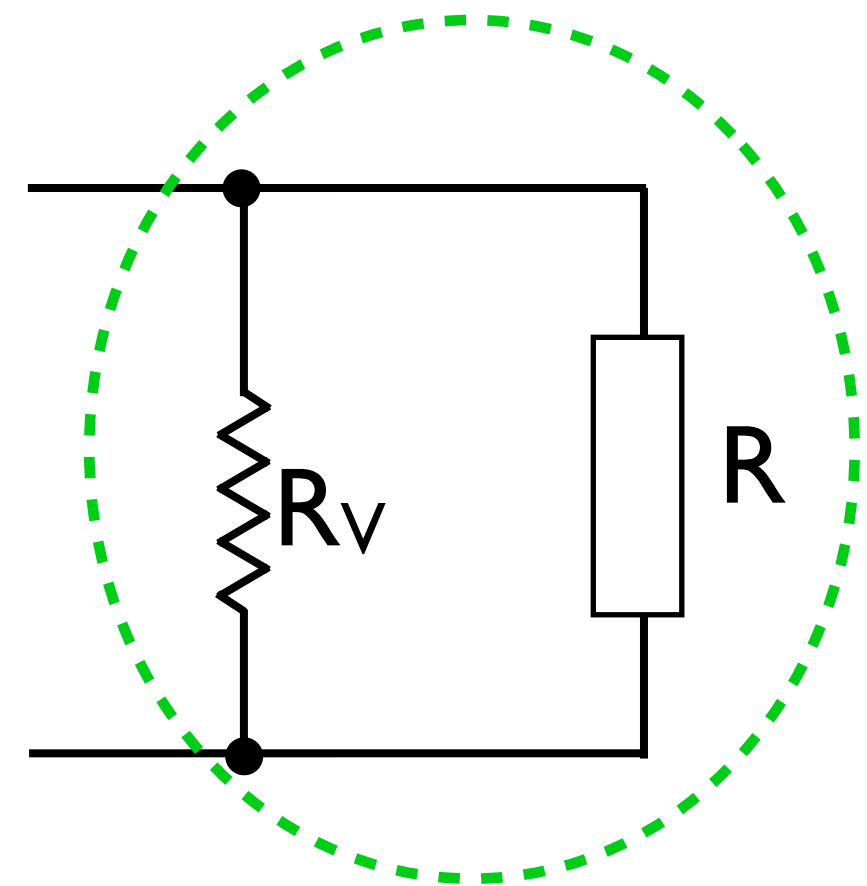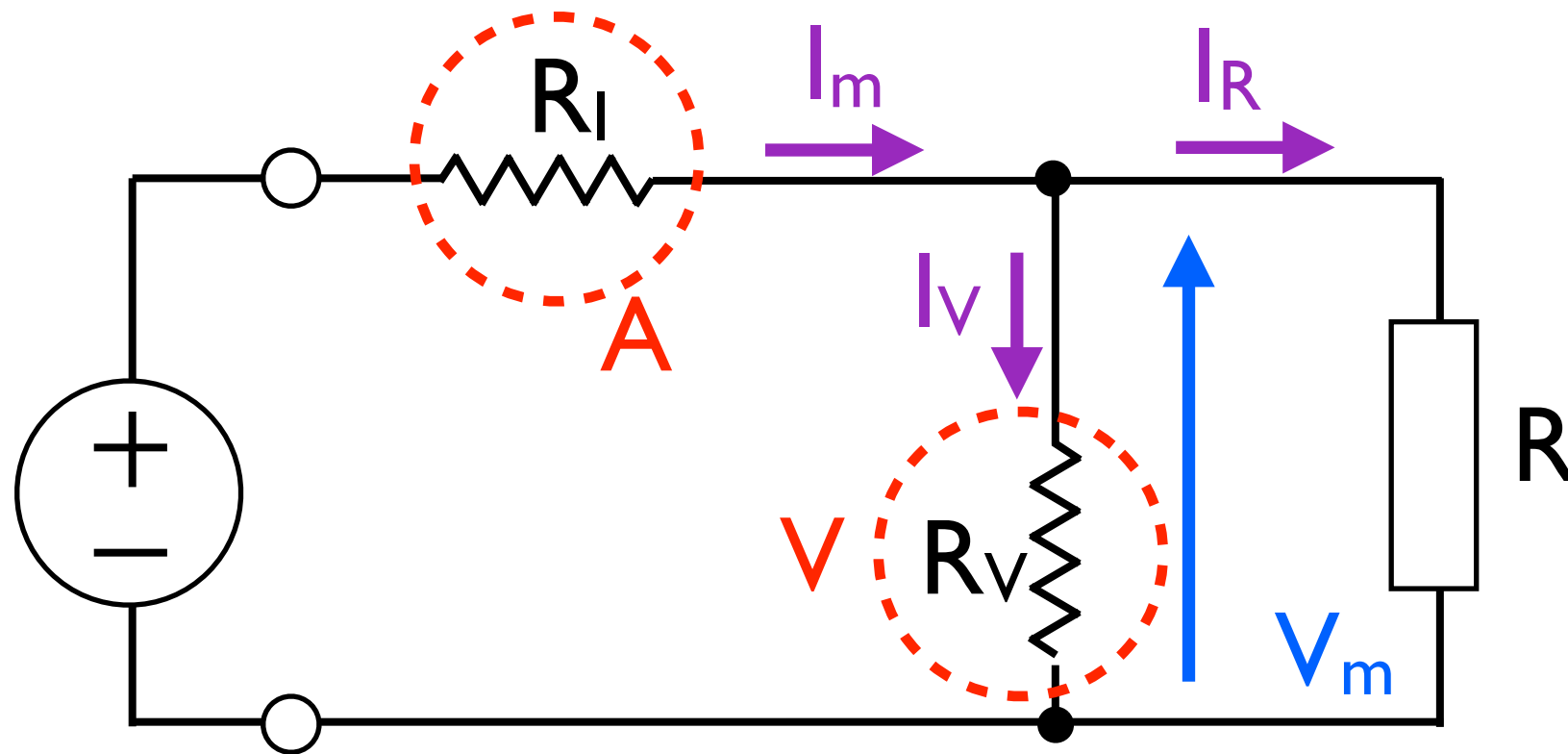


what you
measure

$$\frac{V_m}{I_m} = \frac{I}{I/R - I/R_v}$$

Correction of measured value

$$R = \frac{V_m}{I_m - I_v} = \frac{V_m}{I_m - V_v/R_v}$$

MEASUREMENT OF LOW RESISTANCE

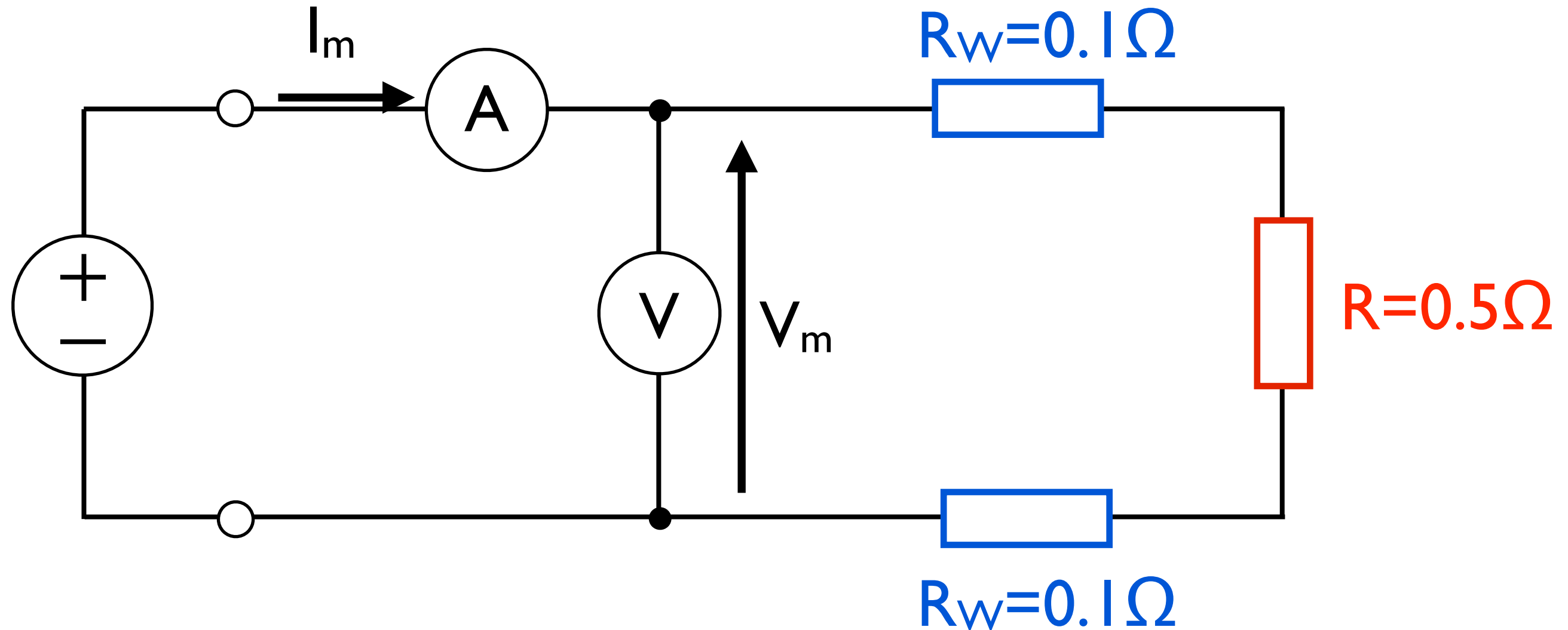


Resistance of cables
and contacts

We actually measure $V_m/I_m = R + 2R_w$

MEASUREMENT OF LOW RESISTANCE

Four wire method

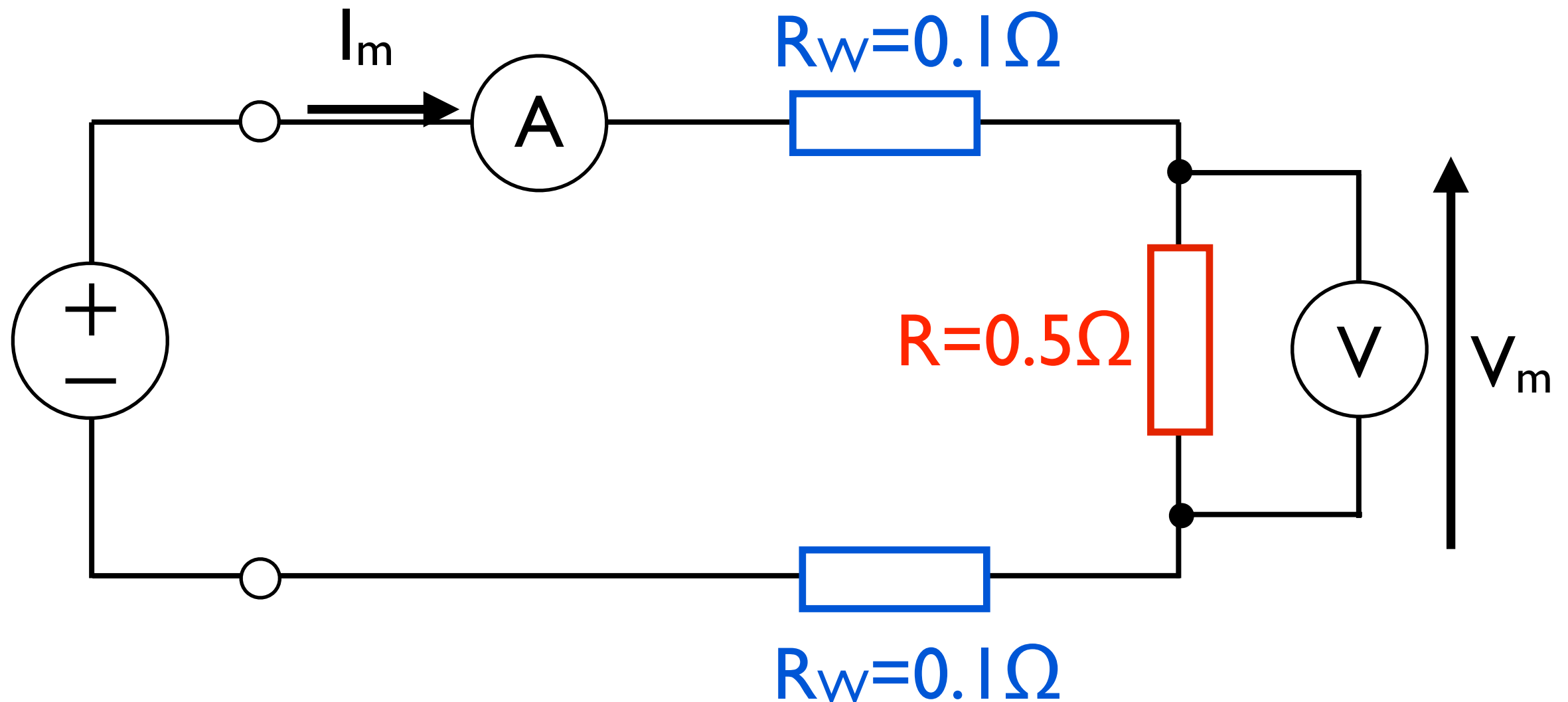


In this case we measure $V_m / I_m = R$

MEASUREMENT OF LOW RESISTANCE



Four wire method

What about the cables of the voltmeter?

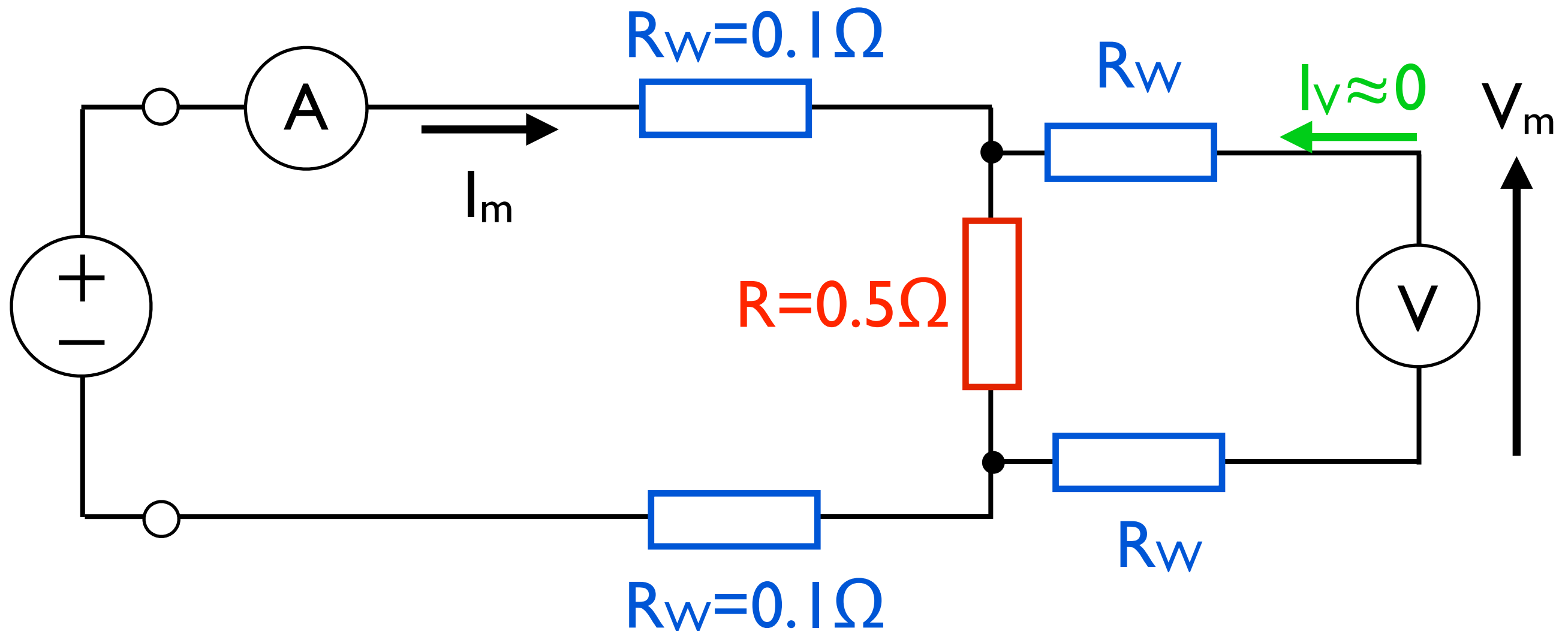



The voltage drop on R_w is negligible because $I_v \approx 0$

MEASUREMENT OF LOW RESISTANCE

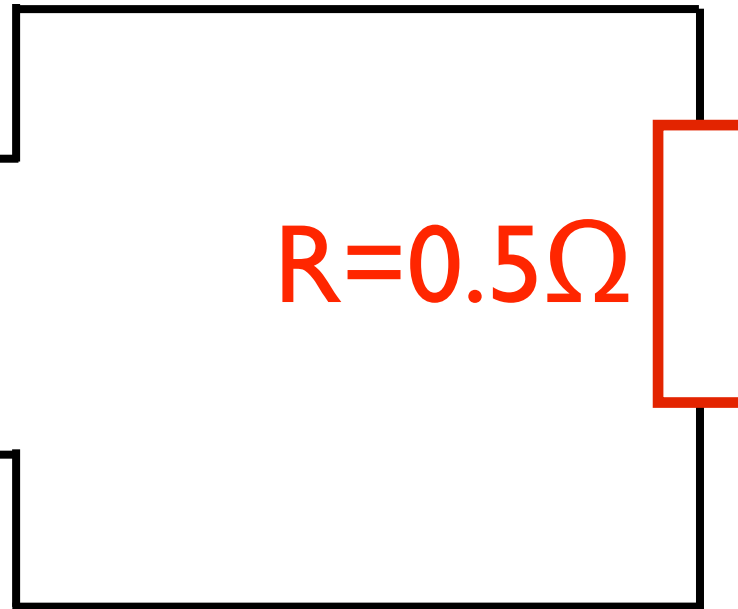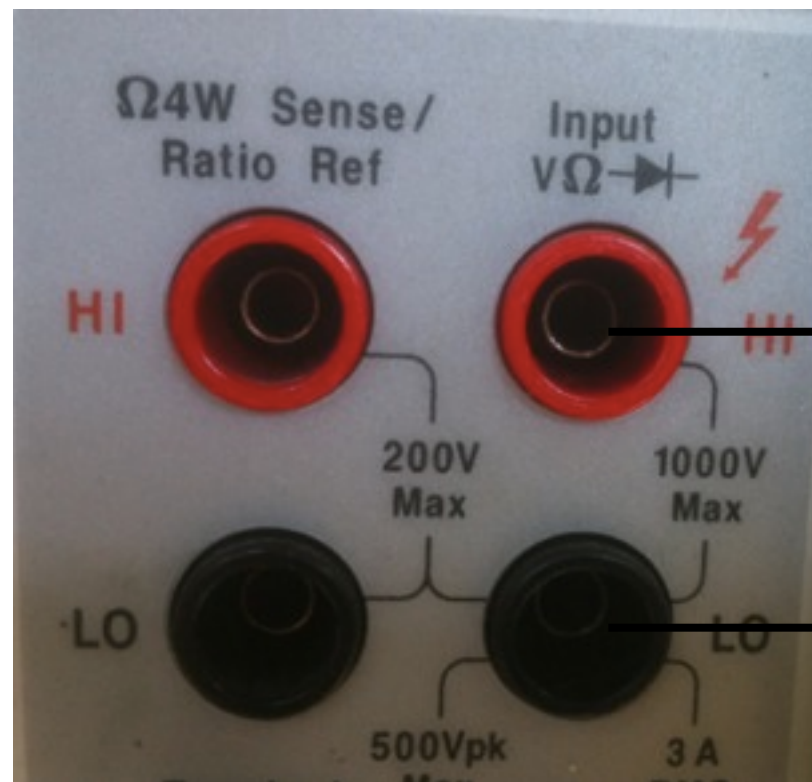


$$R=0.5\Omega$$

Two wire method

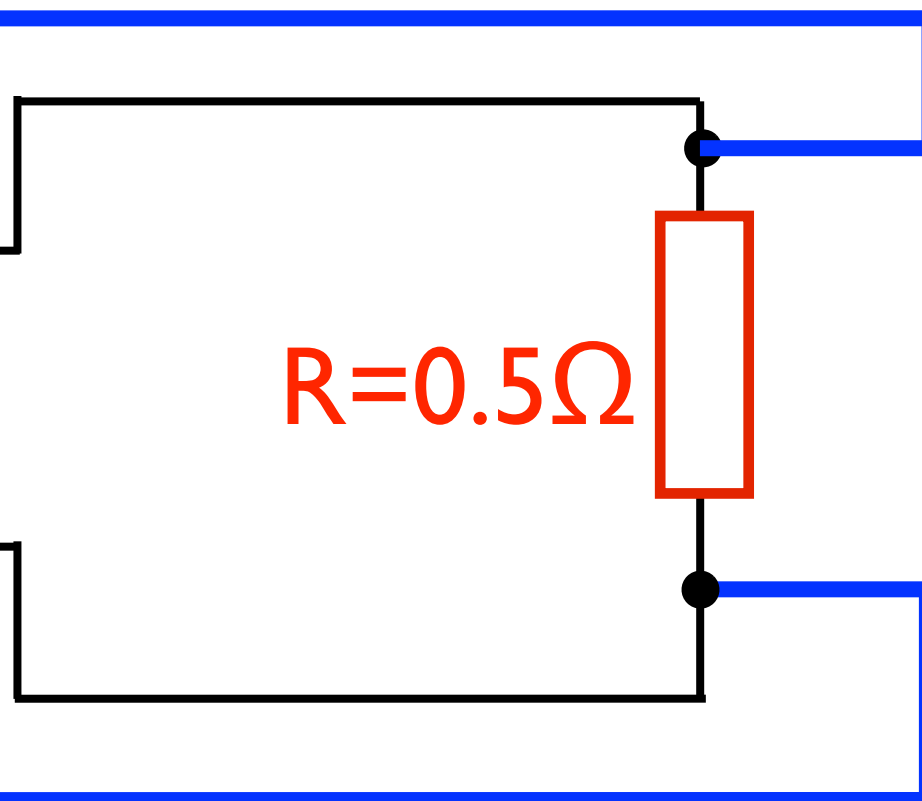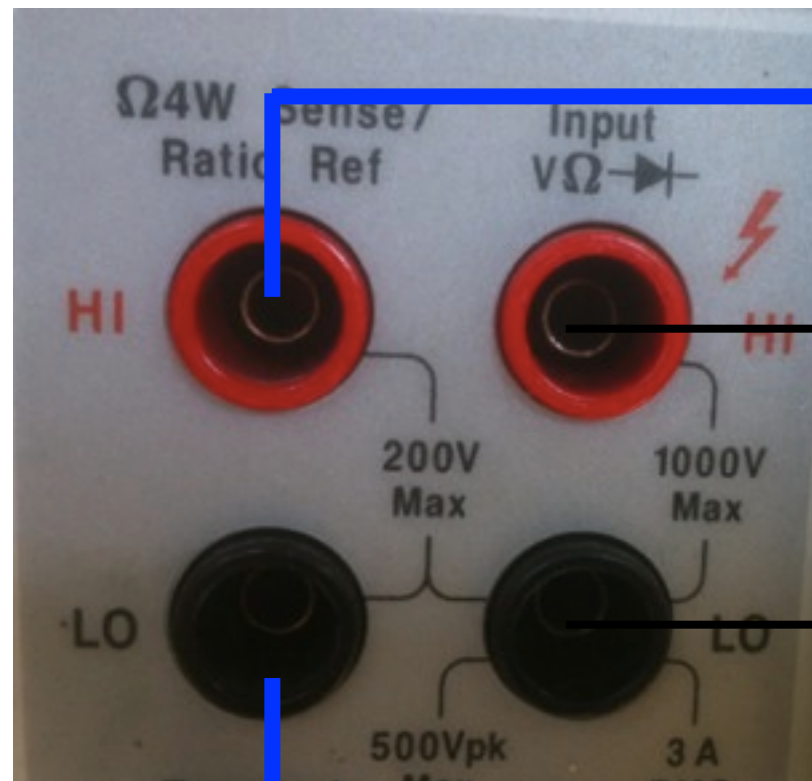

$$R=0.5\Omega$$

Four wire method

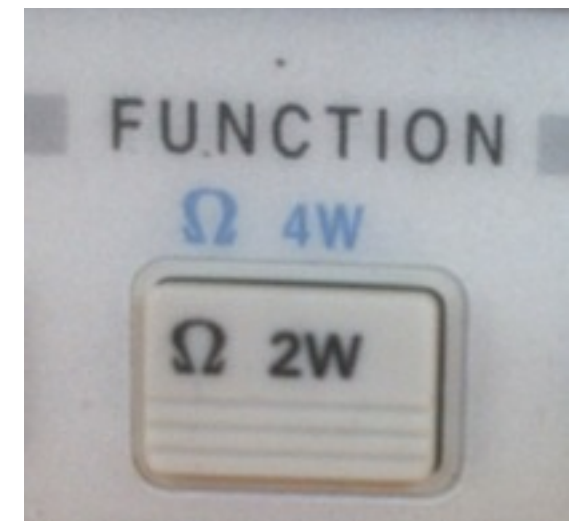


What if the resistance is very, **very low**?

*We should use large current to obtain an acceptable voltage.
Often, it's a problem to measure a large current*

By using COMPARISON METHOD we do not need to
measure the current anymore

COMPARISON METHOD

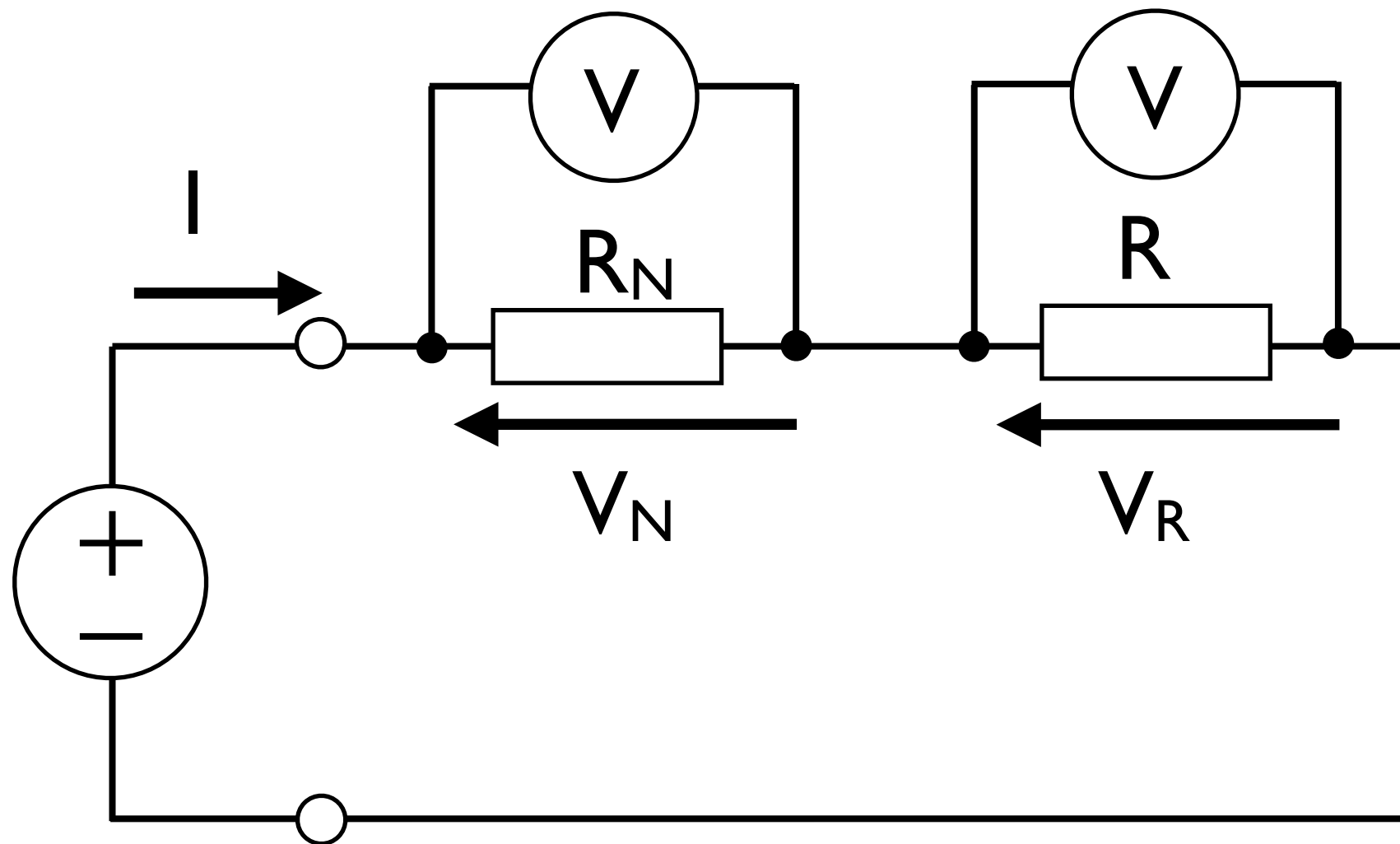

$V_N = R_N \cdot I$ $V_R = R \cdot I$ both resistors share the same current

$$\frac{V_R}{V_N} = \frac{R \cdot I}{R_N \cdot I} = \frac{R}{R_N}$$

$$R = \frac{V_R}{V_N} \cdot R_N$$

COMPARISON METHOD

$$R = \frac{V_R}{V_N} \cdot R_N$$

Sources of uncertainty are only the measured voltages and the standard resistor

STANDARD RESISTORS

PRIMARY standards

*Quantum Hall
effect*

SECONDARY standards

*Wire ($> 1\ \Omega$) of sheet ($< 1\ \Omega$)
of alloy with low temperature
coefficient*

For AC: quadrifilar resistors

SECONDARY STANDARDS




Accuracy: 0.01%



Two connectors
per terminal




QUADRIFILAR STANDARDS

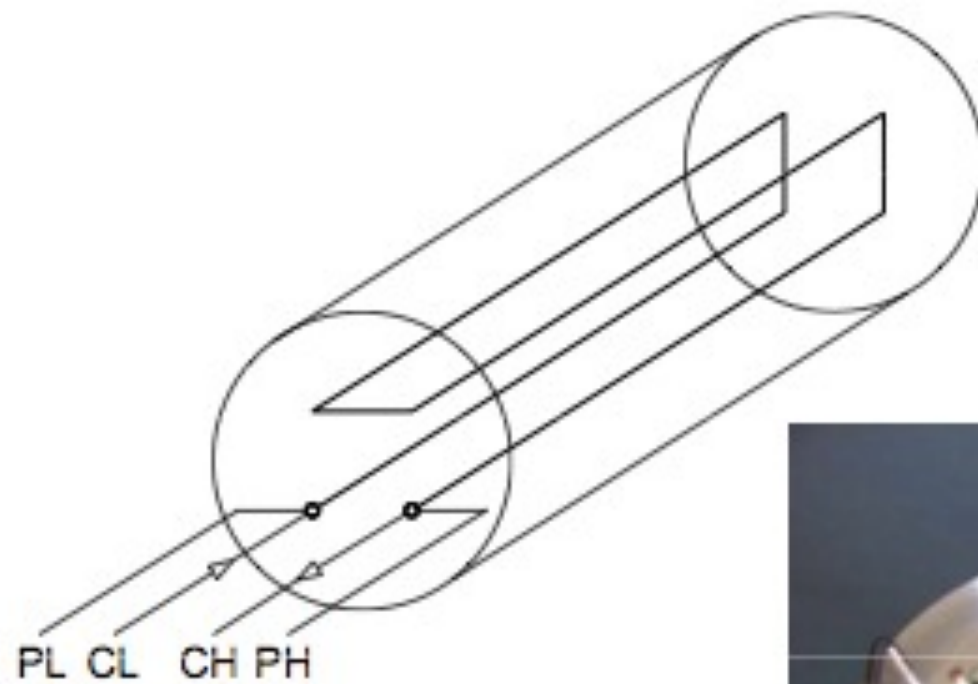

PRIMARY STANDARDS

Classical Hall effect

$$V = k \cdot F = k \cdot I \cdot B$$

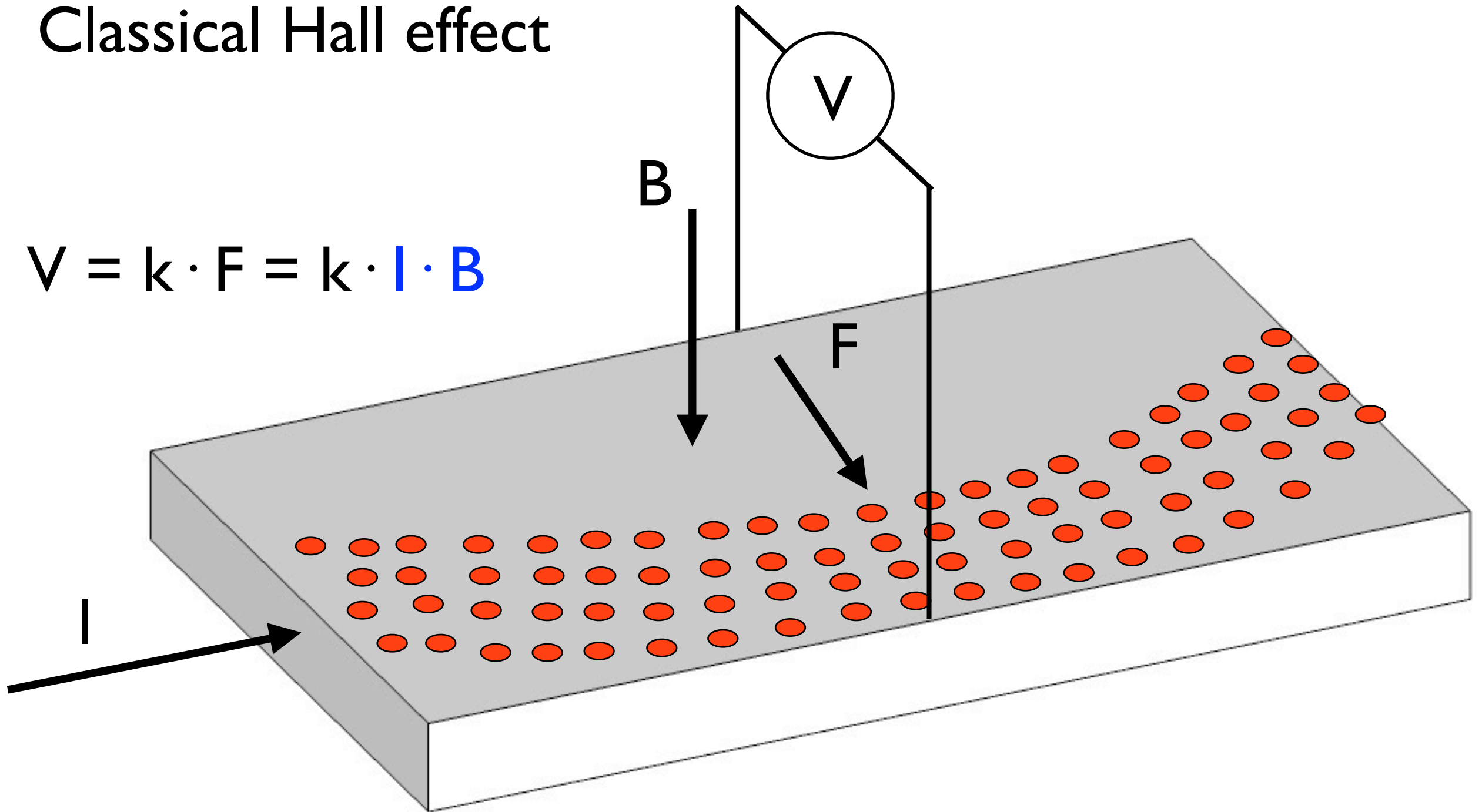

Hall resistance

$$R_H = V / I = k \cdot B$$


Linear to B

PRIMARY STANDARDS

Quantum Hall effect

- very low temperature
- very high magnetic field

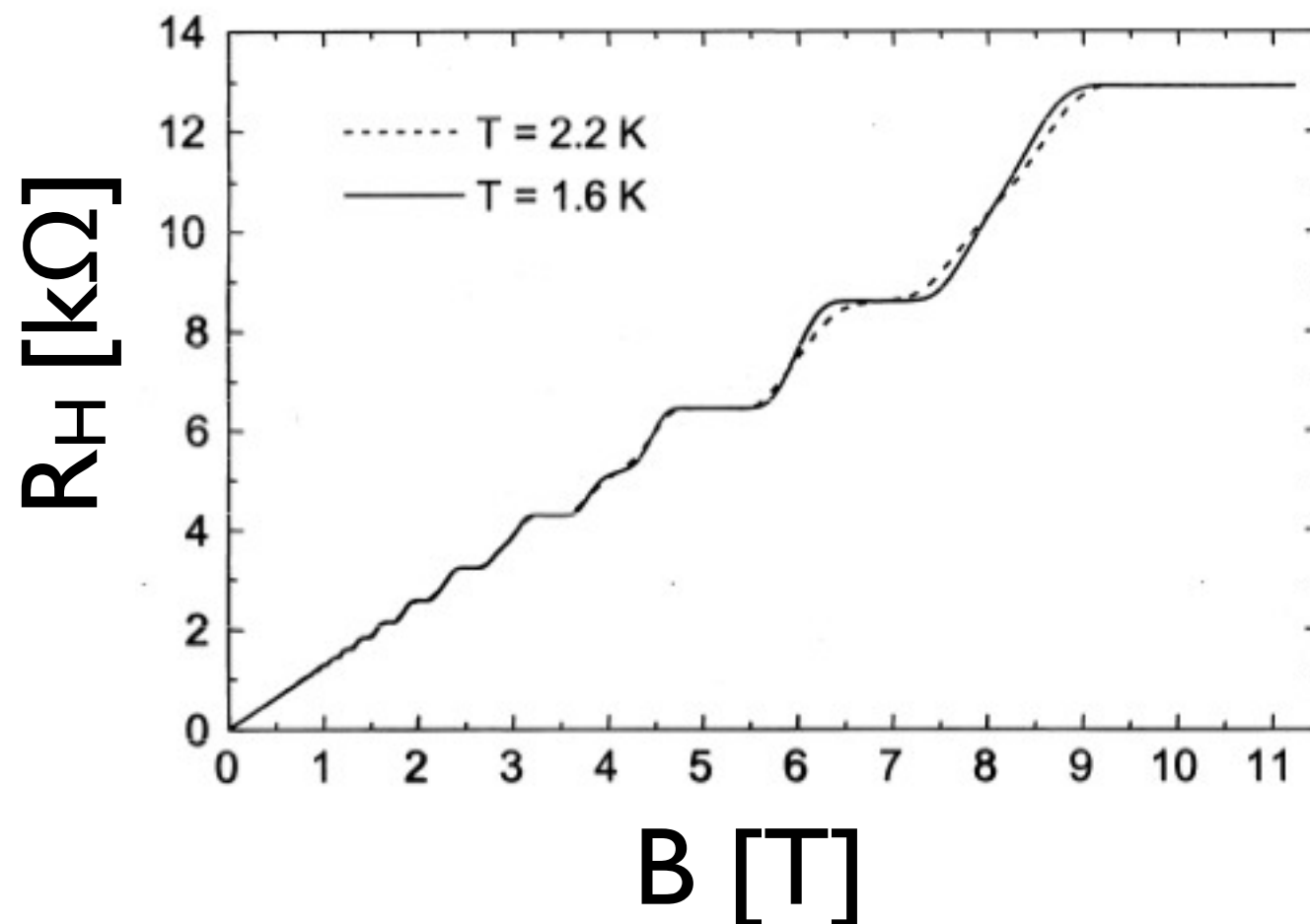The Hall resistance is not linear to B but quantized





Steps of resistance at:

$$R_H = \frac{I}{i} \cdot \frac{h}{e^2}$$


$$R_H = \frac{I}{i} \cdot 25812.8\Omega$$

MEASUREMENT OF LARGE RESISTANCE

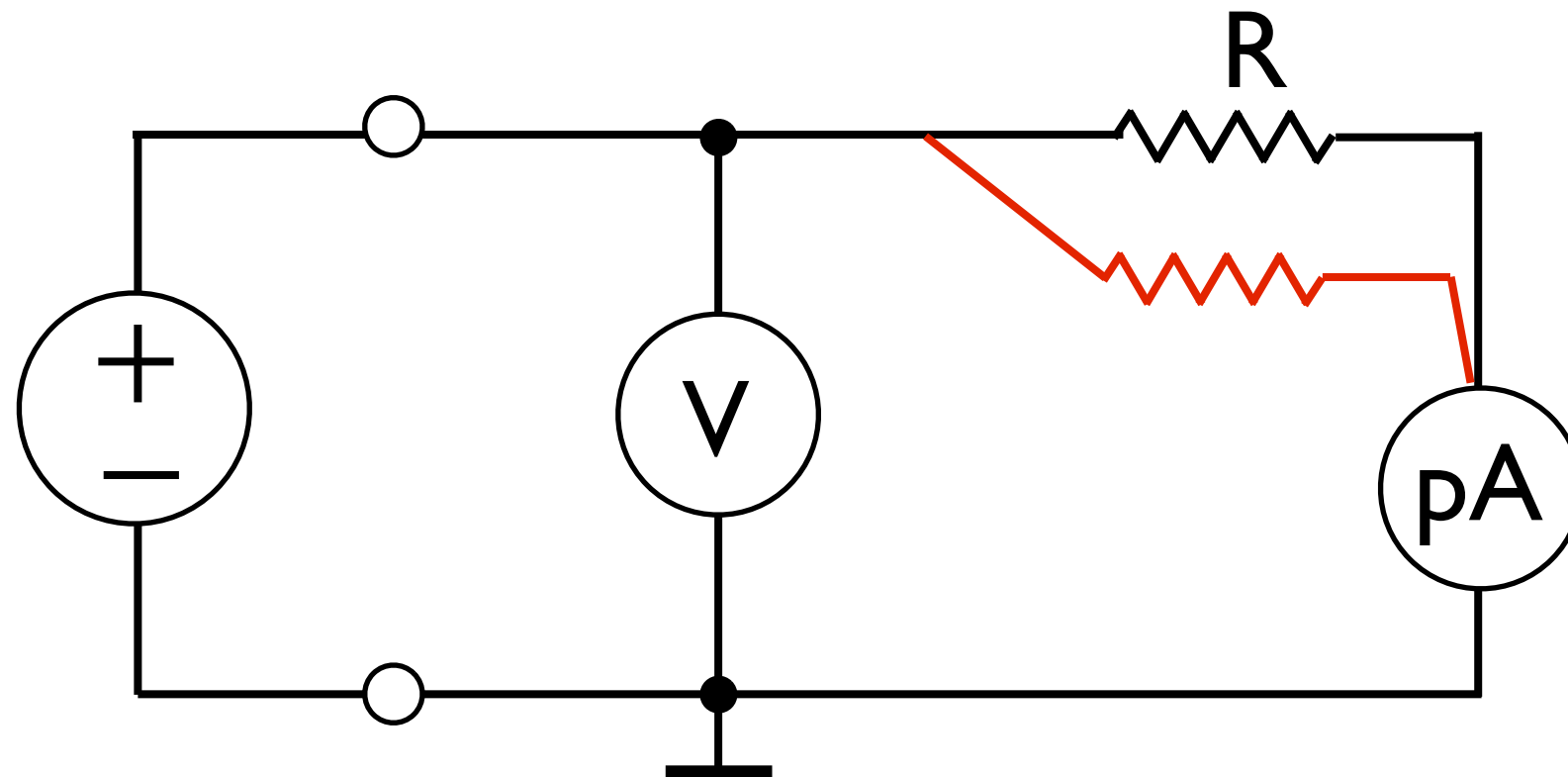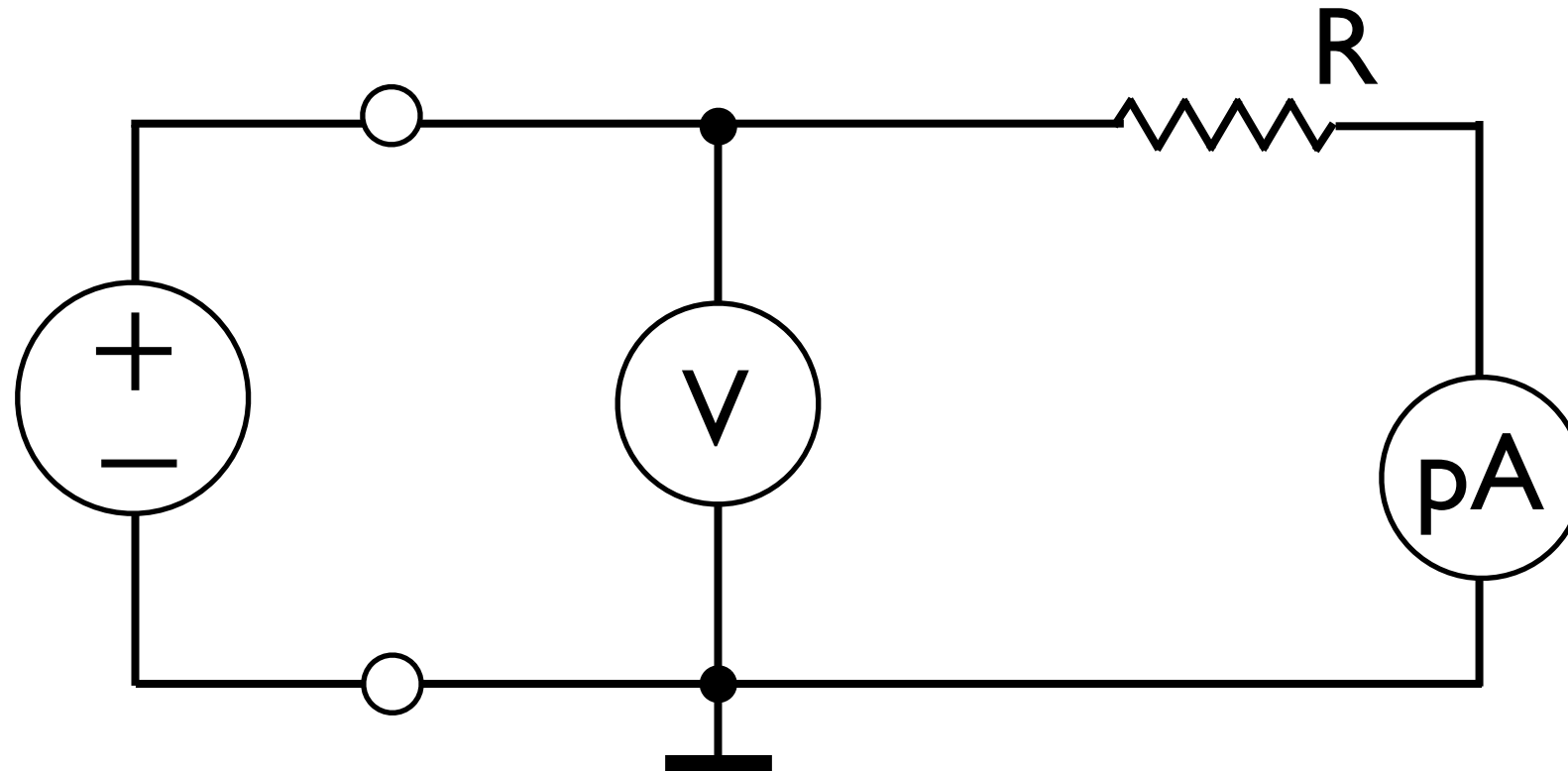


Resistance of insulation might bias pAmmeter

MEASUREMENT OF LARGE RESISTANCE

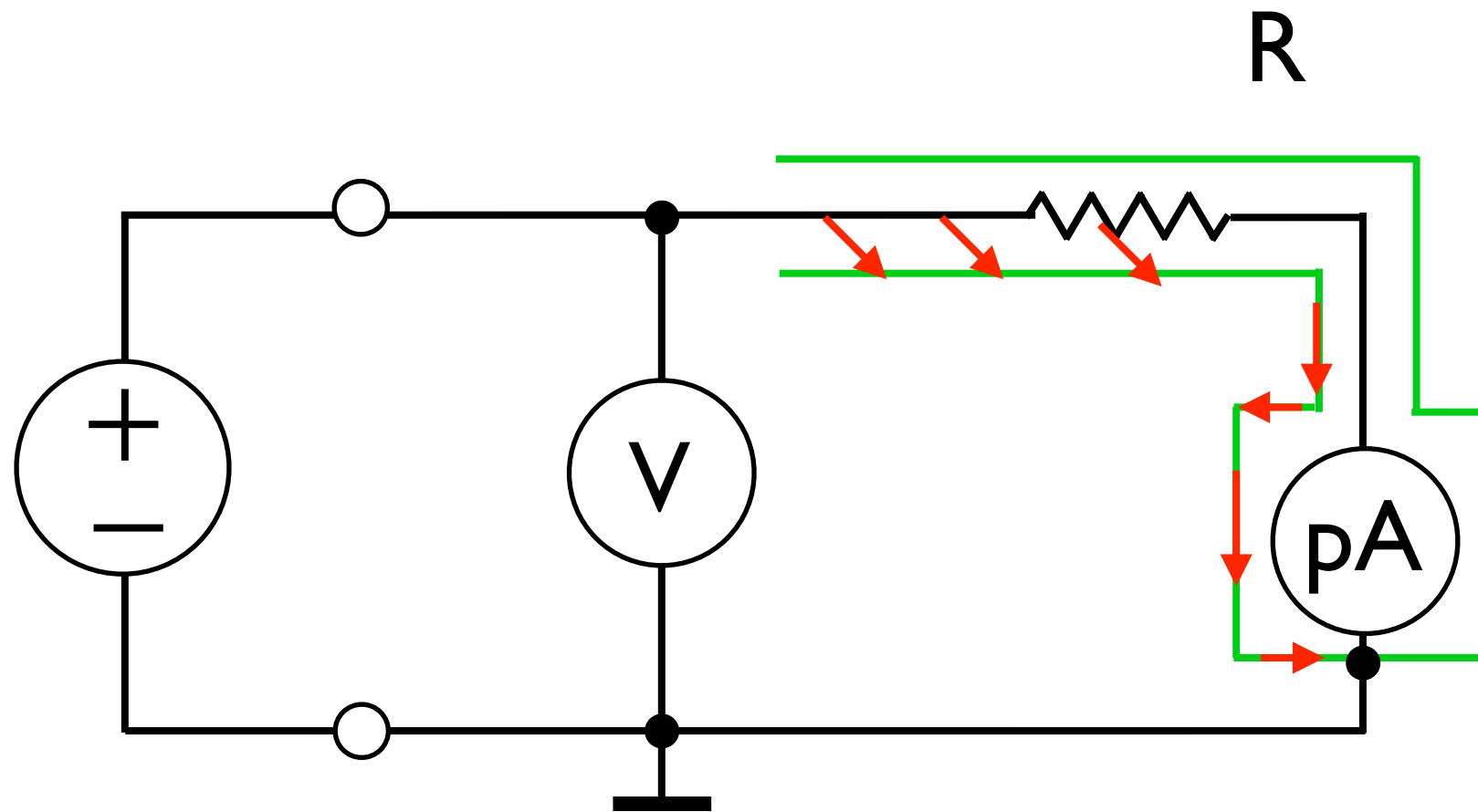

The current flows through the shield instead of loading the pAmmeter

RESISTANCE TO VOLTAGE CONVERTER

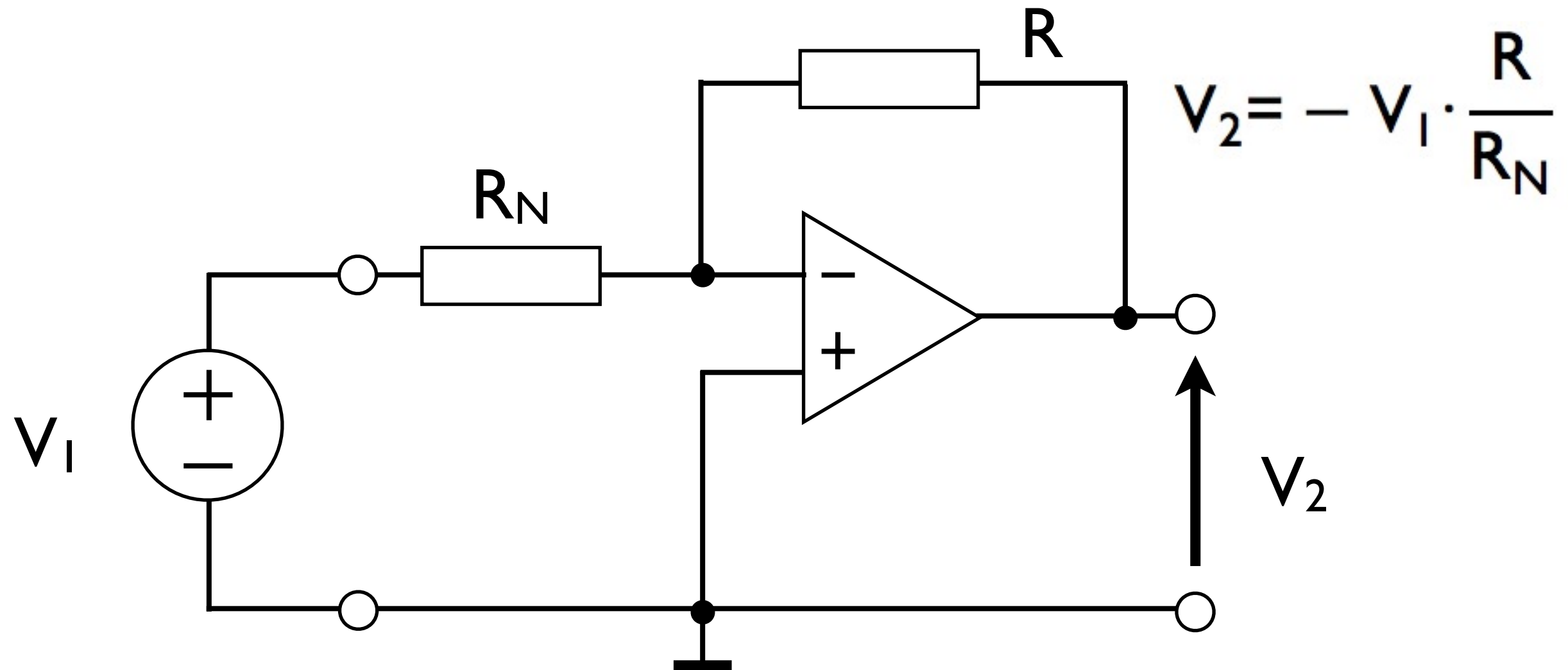

Both V_1 and R_N are constant, so the output V_2 depends only on R

$$R = -\frac{V_2}{V_1} \cdot R_N = k \cdot V_2$$

RESISTANCE TO VOLTAGE CONVERTER

$$R = -\frac{V_2}{V_1} \cdot R_N$$

Sources of uncertainty: V_1, V_2, R_N

Derivates to all variables


$$V_1: \frac{dR}{dV_1} = -\frac{V_2}{V_1^2} \cdot R_N$$

$$V_2: \frac{dR}{dV_2} = -\frac{1}{V_1} \cdot R_N$$

$$R_N: \frac{dR}{dR_N} = -\frac{V_2}{V_1}$$

$$u_R = \sqrt{\left(-\frac{V_2}{V_1^2} \cdot R_N \cdot u_{V_1}\right)^2 + \left(-\frac{1}{V_1} \cdot R_N \cdot u_{V_2}\right)^2 + \left(-\frac{V_2}{V_1} \cdot u_{R_N}\right)^2}$$

R to V converter for **LOW RESISTANCE**

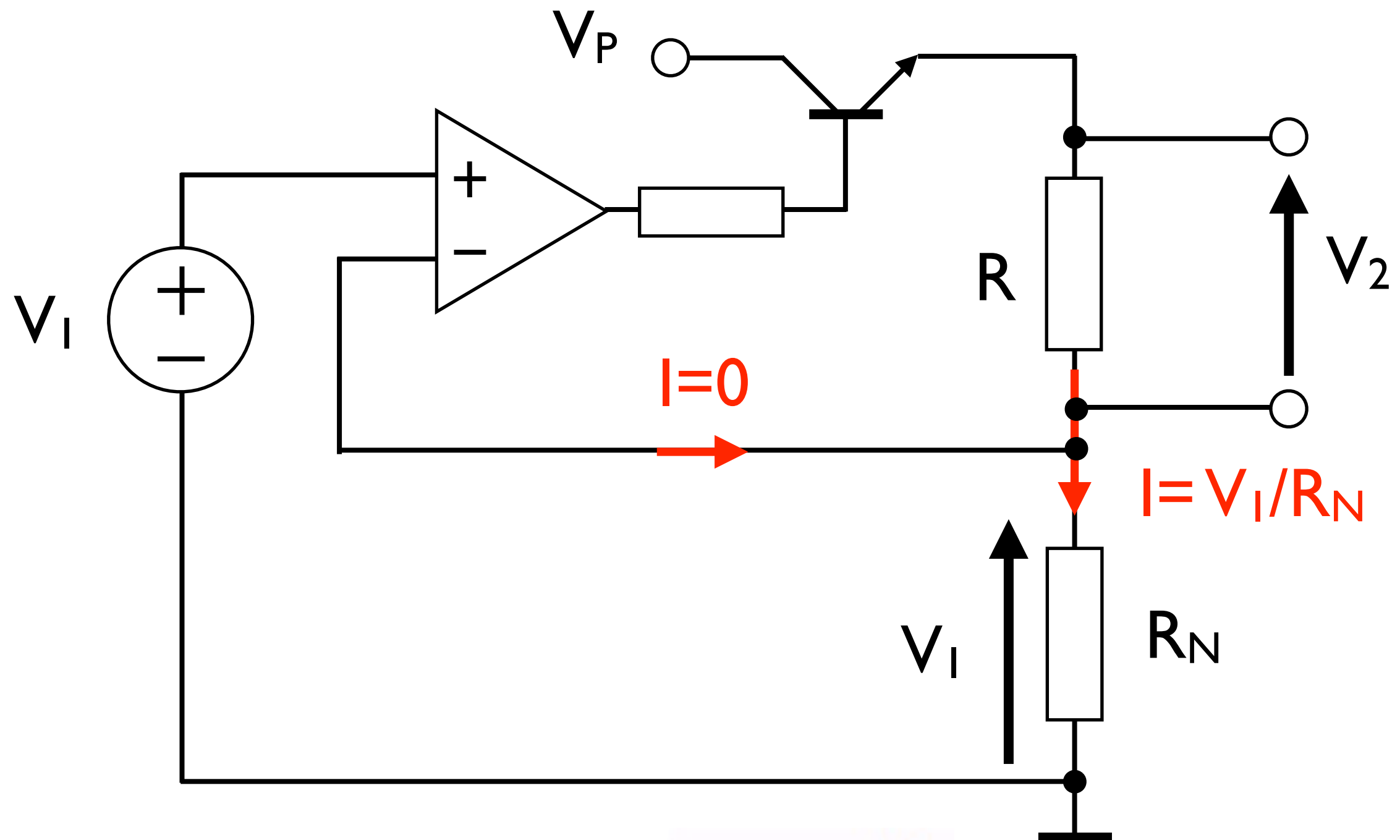

$$V_2 = R \cdot \frac{V_I}{R_N}$$




$$R = R_N \cdot \frac{V_2}{V_I}$$

MEASUREMENT OF RESISTANCE

with large idle value and little changing value

Strain gage

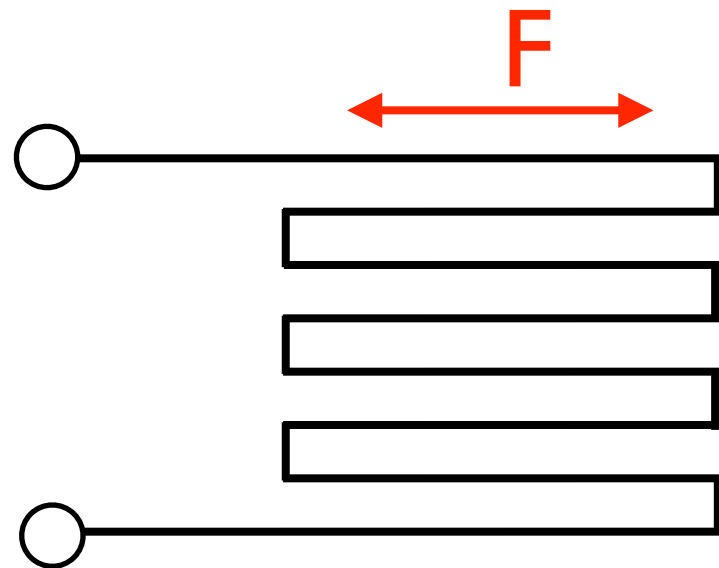

119.95 Ω

⋮

120.05 Ω

If you use a 5 digit ohmmeter you will have only 1 digit resolution, whereas the first 4 digits are “wasted”

119.95 Ω

⋮


120.05 Ω

We must get rid of 120 Ω
and measure only 0.05 Ω

We cannot amplify! Because the big idle value would saturate the instruments. First we must remove 120 Ω , then we can amplify.

Solution:

WHEATSTONE BRIDGE

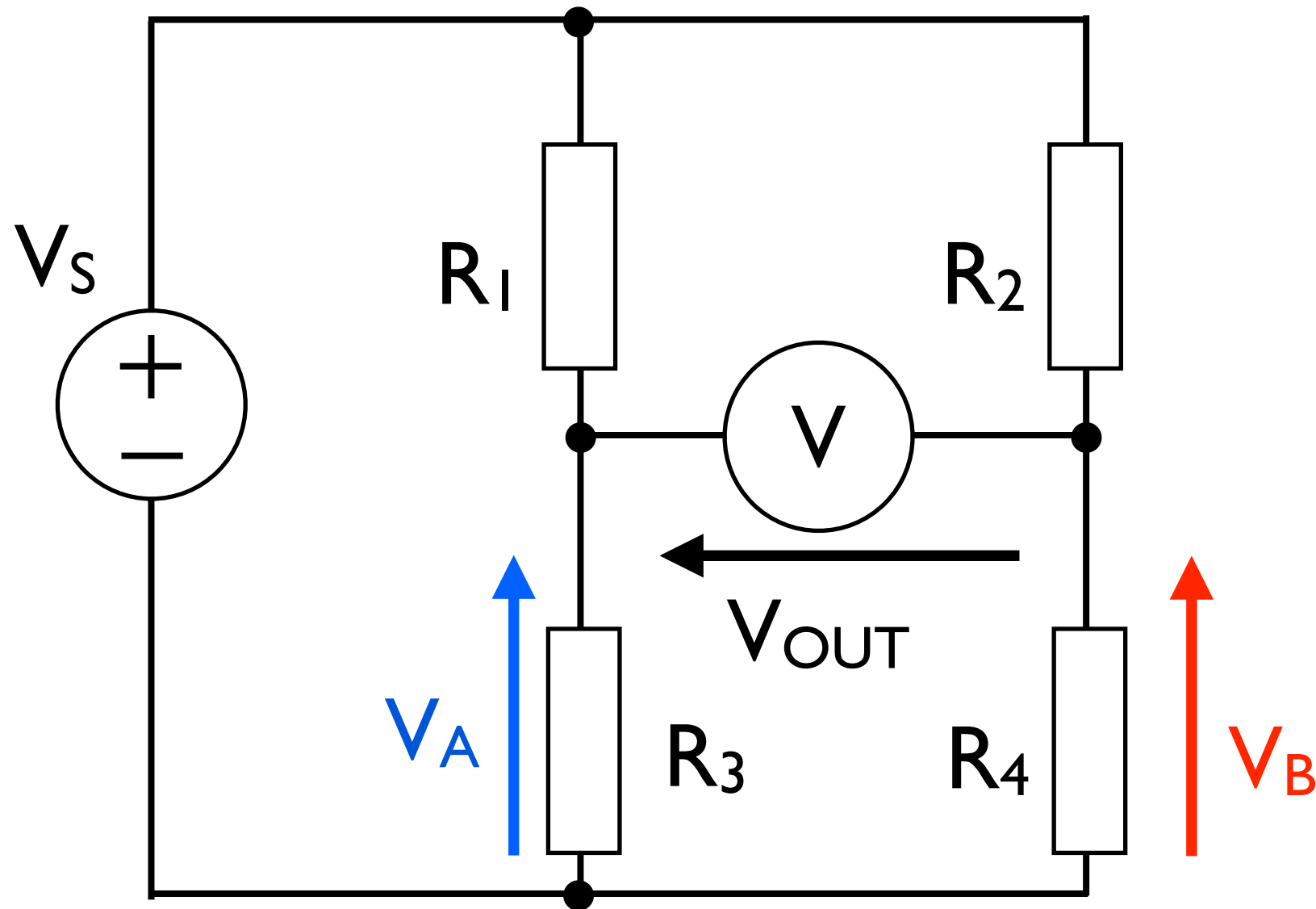

Balanced if:

$$V_{OUT} = 0$$


$$V_A = V_B$$

$$\frac{R_3}{R_1 + R_3} \cdot V_s = \frac{R_4}{R_2 + R_4} \cdot V_s$$

$$\frac{R_3}{R_1 + R_3} = \frac{R_4}{R_2 + R_4}$$

$$R_2 \cdot R_3 = R_1 \cdot R_4$$

WHEATSTONE BRIDGE

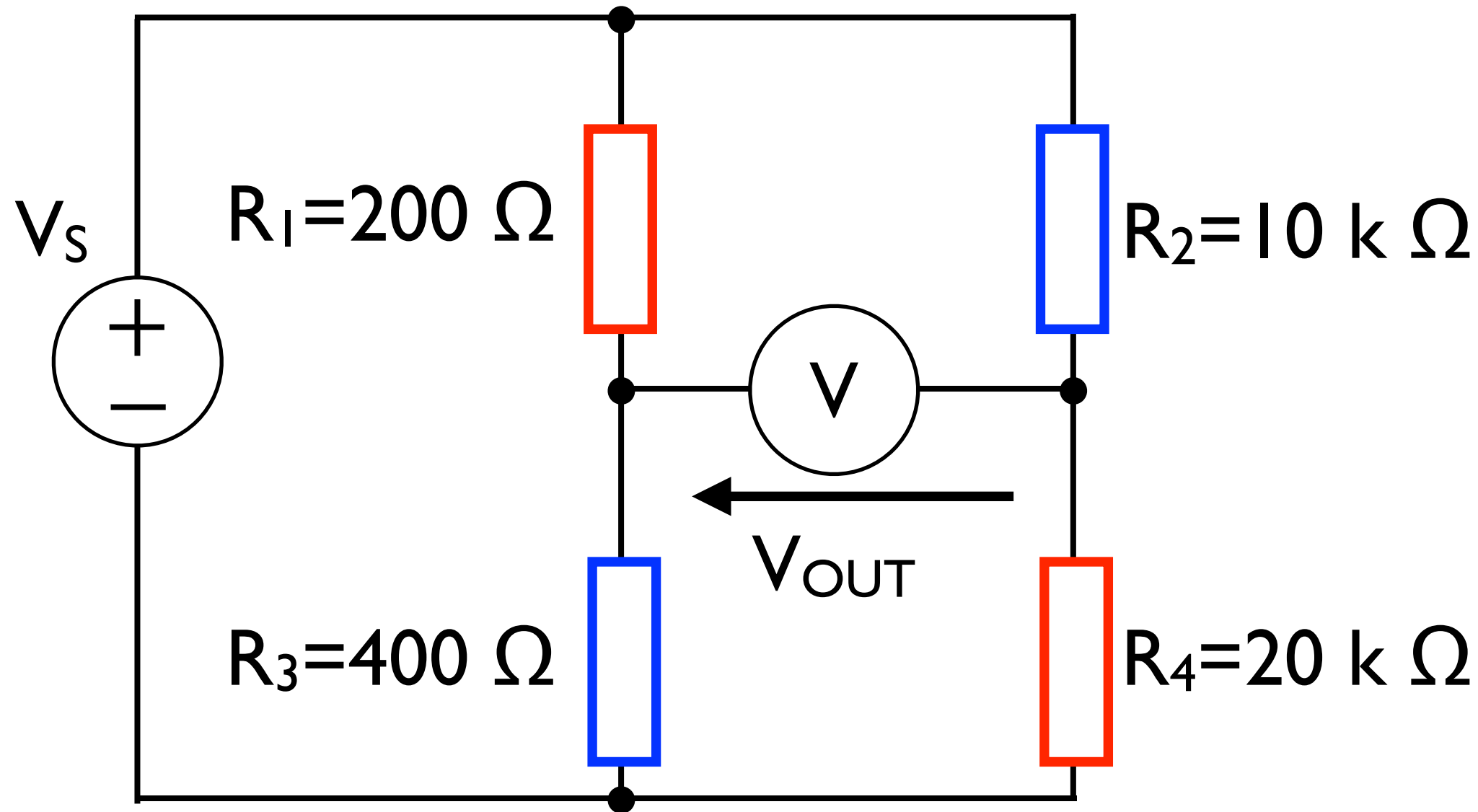


$$R_2 \cdot R_3 = R_1 \cdot R_4$$

$$10,000 \cdot 400 = 200 \cdot 20,000$$

WHEATSTONE BRIDGE

Unbalanced bridge

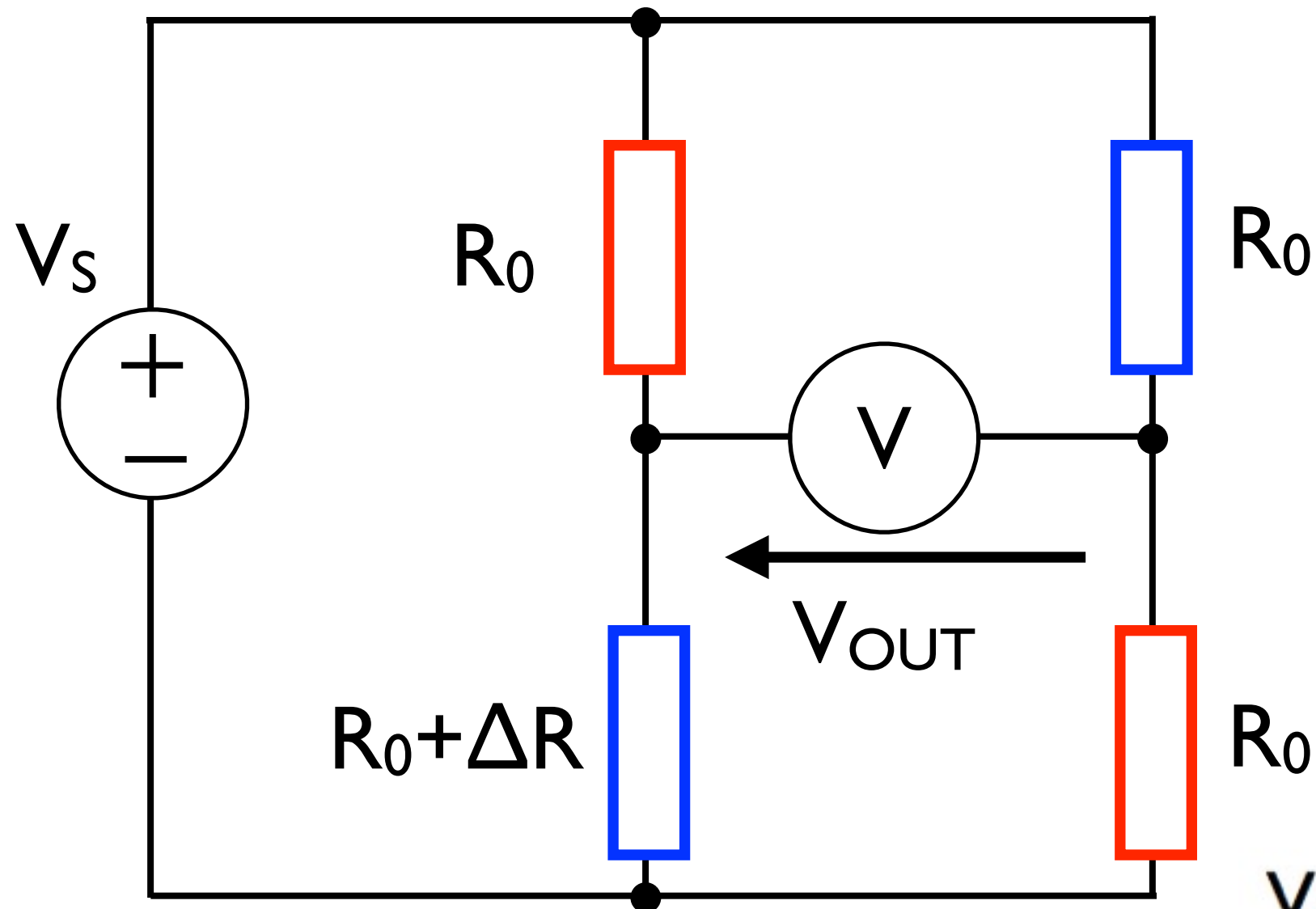

Let us assume all resistance to be nominally equal to R_0


Linear only for $\Delta R \ll R_0$

$$V_{OUT} = \left(\frac{R_0 + \Delta R}{2 \cdot R_0 + \Delta R} - \frac{1}{2} \right) \cdot V_S$$

$$V_{OUT} = \frac{\Delta R}{4 \cdot R_0 \left(1 + \frac{\Delta R}{2 \cdot R_0} \right)} \cdot V_S$$

WHEATSTONE BRIDGE

Controlled bridge

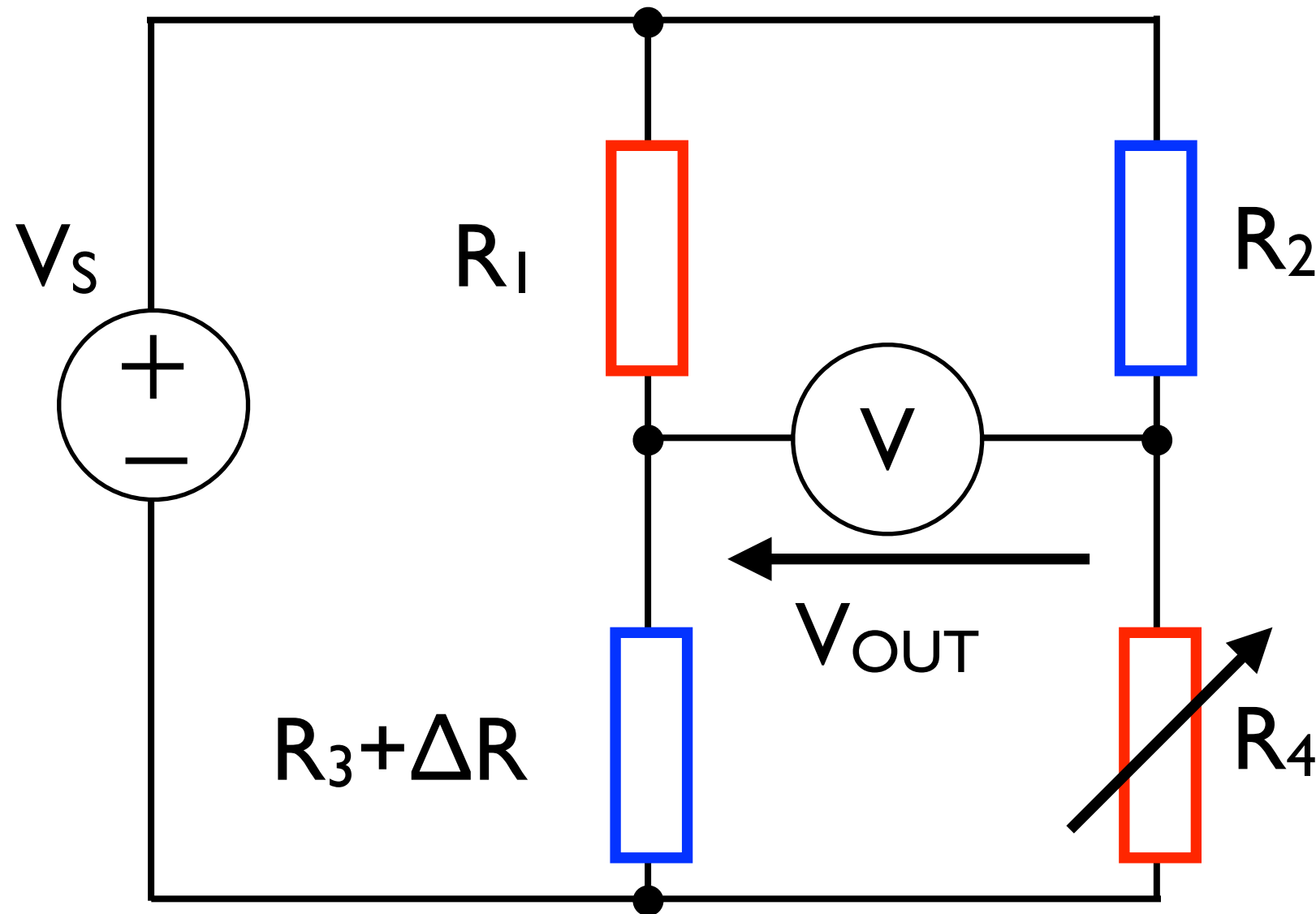

I change the value of R_4 until $V_{OUT}=0$ in order to restore the balanced condition

$$R_2 \cdot R_3 = R_1 \cdot R_4$$

Then, R_4 - which is known - equals $R_3 + \Delta R$